

- Internal Battery **Voltage** = 3.6V
- Output **Voltage** = 5.1V (Via V boost/buck circuit)
- Output **Current** = 2.1A x 2 Channel (But sum max = 3.6A)
- Output **Power** =  $5.1 \times 2.1 = 10.71$  Watts
- Energy Capacity (at 5.1V) = 10200 mAh  
=  $10200 \times 5.1 = 52.02$  Wh



S20 ultra Battery Capacity  
5000 mAh x 3.86V = 19.30 Wh

Phone supports 45W charging.  
In theory it can charge from 0% to 100% in

$$19.30/45 = 0.43 \text{ hrs (25.8 min)}$$

BUT wait ...



You also need the following:

Charger that

- Supports PD 3.0, PPS 2.0
- Supports 10V/4.5A
- E-marked USB-C Cable



- เอาต์พุต Type-C: 5 V/3A, **9 V/3A**, 12 V/3A, 14.5 V/3A, 20 V/3A (PD60W Max)
- เอาต์พุต USB-A1: 5 V/2.4A
- เอาต์พุต USB-A2: 5 V/2.4A



Most likely get this power output  
 $9 \times 3 = 27$  Watt

Type-C cable must also handle  
this power


# Power Supply?



USB 3.0



USB 2.0

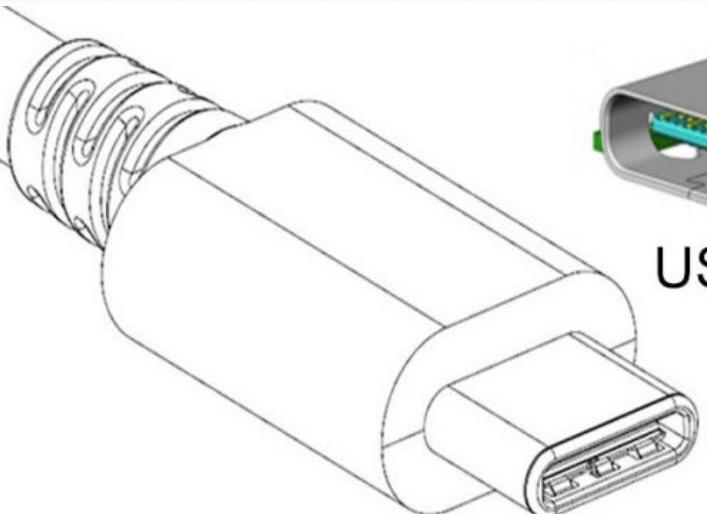

USB Type-C  
Reversible

Max. current	0.5 A (USB 2.0) 0.9 A (USB 3.0 & 3.1) 3 A (USB Type-C)
--------------	--

# Other types of batteries




**Li-ion (Lithium ion)**  
Rechargeable, High capacity,  
Explode when short circuited



**LIPO (Lithium Polymer)**  
Rechargeable, Very high current (Good for Drones)  
Easily damaged

# What's wrong with this circuit?

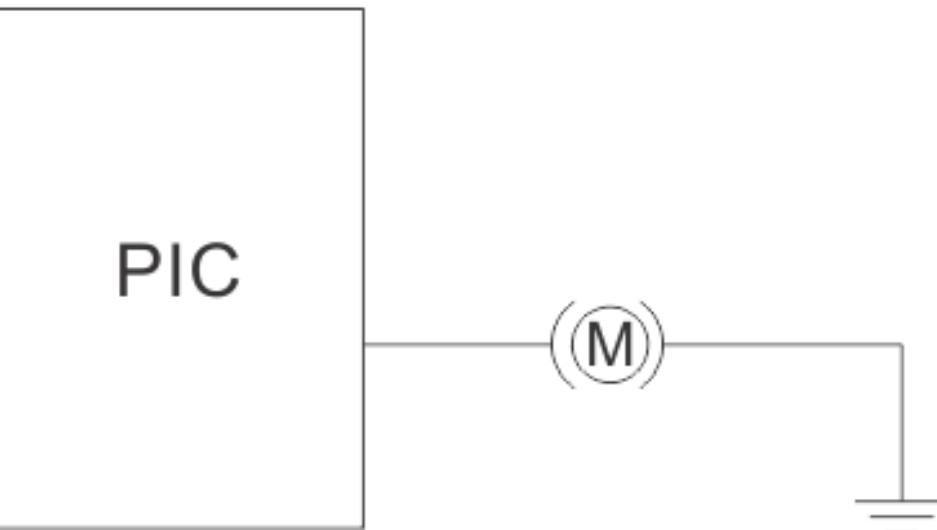


A microcontroller usually supplies limited current (i.e. 25 mA).  
This is ok for LEDs but not enough for high current loads like a motor

# Output Control: Power transfer



Driving an electrical load is essentially about transferring power from the source to the load.



# Output Control: Power transfer

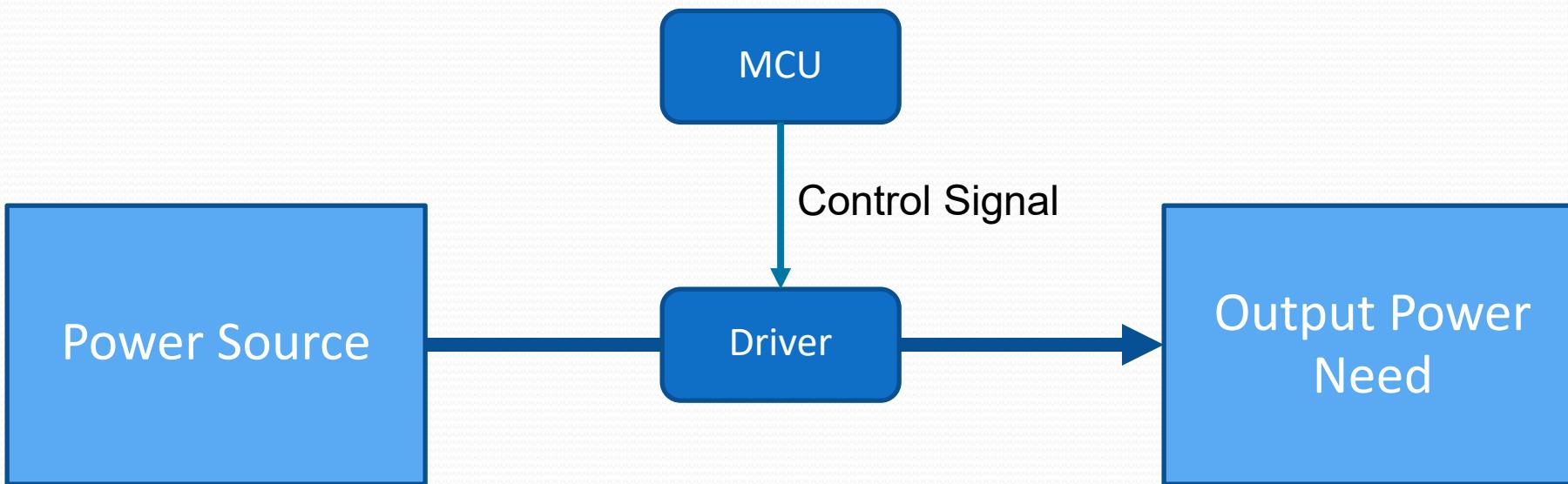


The transfer is done using a “driver” which is a device that, for this course, can be controlled by a micro-controller.

# Transistors

Using transistors as a switch

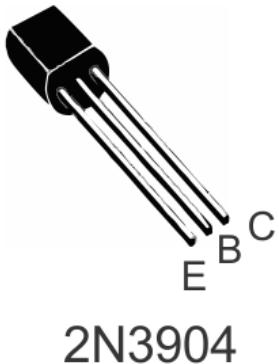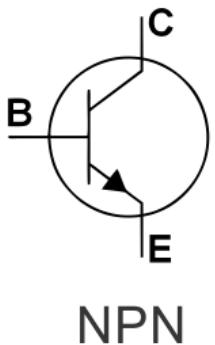


2N3904

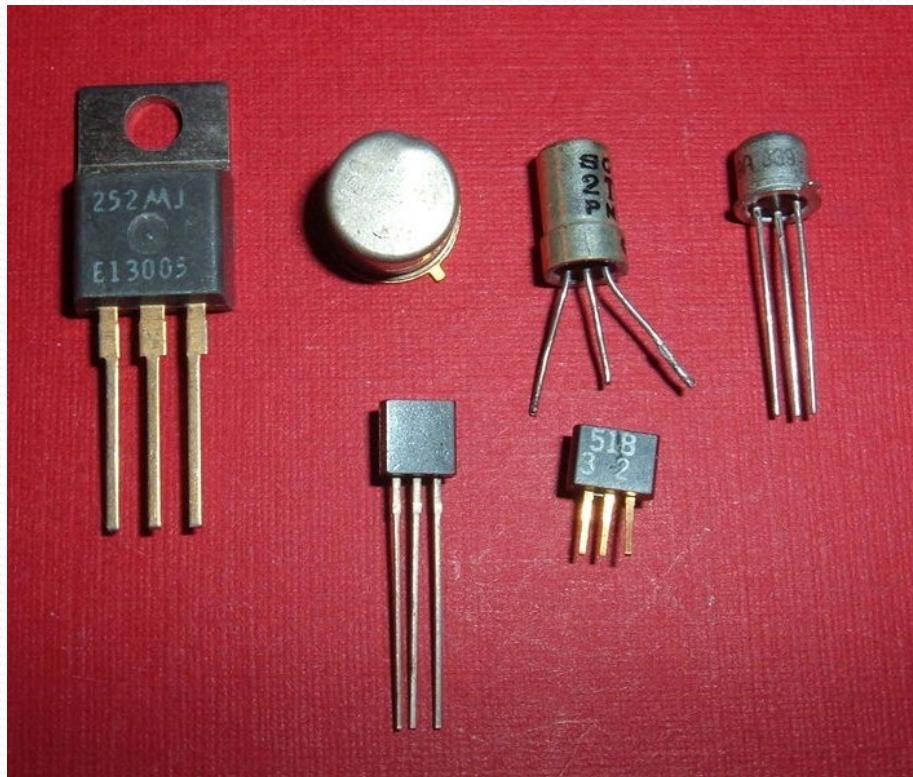

Transistors works both as (1) a switch and (2) a current amplifier.  
Transistors allow us to send higher current to a load.

# Using a transistor

## Low-side switching

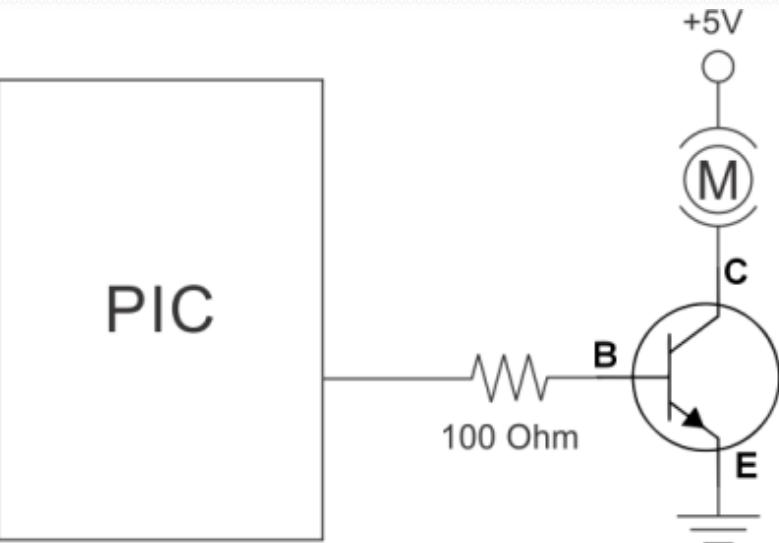

100 Ohm resistor is to limit the amount of current triggering the base

# Different Loads Requires Different Power



Typical LEDs

5-15 mA @5V  
Or 25-75 mW



Small DC Motors

100-200 mA @5V  
Or 0.5-1W



Irrigation Control Valve

0.6-1.0 A @24V  
Or 14-24W

# Calculate the Power Parameters



0.6-1.0 A @24V



Voltage = 24V

Current = 0.6-1.0A

Power =  $24 \times 1 = 24W$

Energy = Power \* Time

# Can the 2N3904 control the valve?

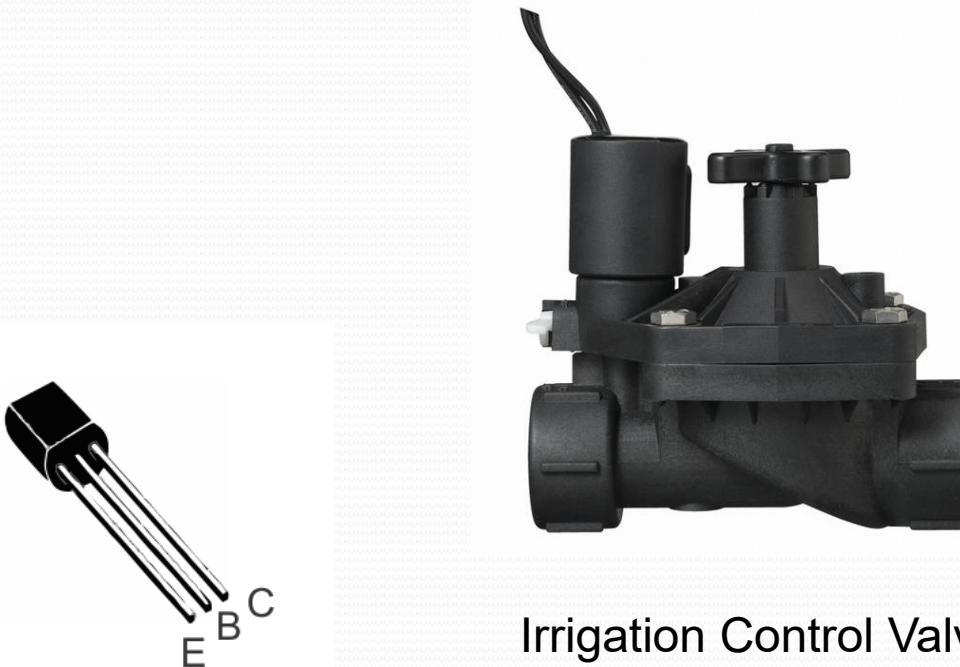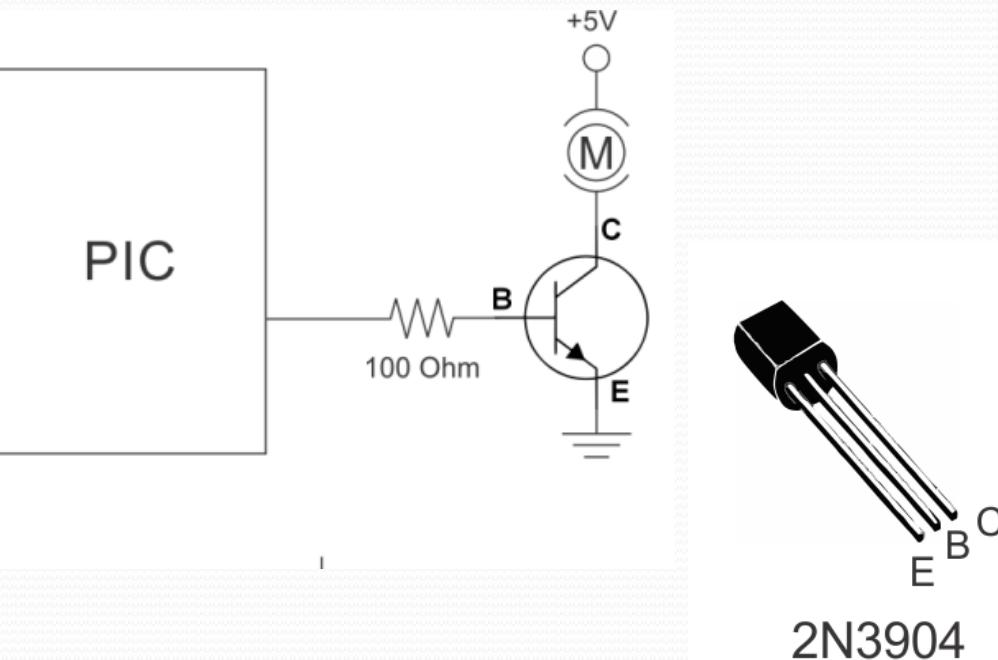


Irrigation Control Valve

0.6-1.0 A @24V  
Or 14-24W

# The answer is in the datasheet

## ABSOLUTE MAXIMUM RATINGS

Symbol	Parameter	Value	Unit
$V_{CBO}$	Collector-Base Voltage ( $I_E = 0$ )	60	V
$V_{CEO}$	Collector-Emitter Voltage ( $I_B = 0$ )	40	V
$V_{EBO}$	Emitter-Base Voltage ( $I_C = 0$ )	6	V
$I_C$	Collector Current	200	mA
$P_{tot}$	Total Dissipation at $T_c = 25^\circ\text{C}$	625	mW
$T_{stg}$	Storage Temperature	-65 to 150	$^\circ\text{C}$
$T_J$	Max. Operating Junction Temperature	150	$^\circ\text{C}$

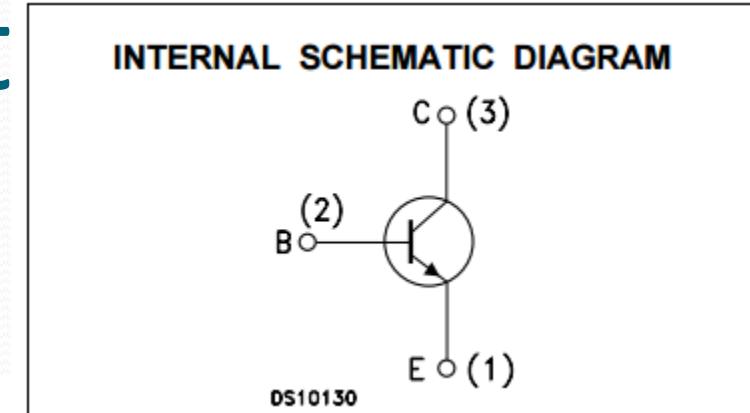

## ABSOLUTE MAXIMUM RATINGS

Symbol	Parameter	Value	Unit
$V_{CBO}$	Collector-Base Voltage ( $I_E = 0$ )	60	V
$V_{CEO}$	Collector-Emitter Voltage ( $I_B = 0$ )	40	V
$V_{EBO}$	Emitter-Base Voltage ( $I_C = 0$ )	6	V
$I_C$	Collector Current	200	mA
$P_{tot}$	Total Dissipation at $T_c = 25^\circ\text{C}$	625	mW
$T_{stg}$	Storage Temperature	-65 to 150	$^\circ\text{C}$
$T_J$	Max. Operating Junction Temperature	150	$^\circ\text{C}$

1. Control 24V? -> Yes

2. Can supply enough current? -> No.

- At 24V, the maximum current is  $625/24 = 26 \text{ mA}$
- Notice that 26 mA is a lot less than 200 mA
- 200 mA can be achieved only at  $625/200 = 3.125 \text{ V}$

# How about this one?



KTD882

## MAXIMUM RATINGS (Ta=25°C)

CHARACTERISTIC		SYMBOL	RATING	UNIT
Collector-Base Voltage		V <sub>CBO</sub>	40	V
Collector-Emitter Voltage		V <sub>CEO</sub>	30	V
Emitter-Base Voltage		V <sub>EBO</sub>	5	V
Collector Current	DC	I <sub>C</sub>	3	A
	Pulse (Note)	I <sub>CP</sub>	7	
Base Current (DC)		I <sub>B</sub>	0.6	A
Collector Power Dissipation	Ta=25°C	P <sub>C</sub>	1.5	W
	Tc=25°C		10	
Junction Temperature		T <sub>j</sub>	150	°C
Storage Temperature Range		T <sub>stg</sub>	-55~150	°C

Note : Pulse Width  $\leq$ 10mS, Duty Cycle $\leq$ 50%.

## MAXIMUM RATINGS ( $T_a=25^\circ\text{C}$ )

CHARACTERISTIC	SYMBOL	RATING	UNIT
Collector-Base Voltage	$V_{CBO}$	40	V
Collector-Emitter Voltage	$V_{CEO}$	30	V
Emitter-Base Voltage	$V_{EBO}$	5	V
Collector Current DC	$I_C$	3	A
Pulse (Note)	$I_{CP}$	7	
Base Current (DC)	$I_B$	0.6	A
Collector Power Dissipation	$T_a=25^\circ\text{C}$	1.5	W
	$T_c=25^\circ\text{C}$	10	
Junction Temperature	$T_j$	150	$^\circ\text{C}$
Storage Temperature Range	$T_{stg}$	-55~150	$^\circ\text{C}$

Note : Pulse Width  $\leq 10\text{mS}$ , Duty Cycle  $\leq 50\%$ .

1. Control 24V? -> Yes
2. Can supply enough current? -> No.

- At 24V, the maximum current is  $10/24 = 0.416 \text{ A}$

$T_a$  = Atmosphere Temperature  
 $T_c$  = Case Temperature

# This one? ST-13005

## ABSOLUTE MAXIMUM RATINGS

Symbol	Parameter	Value	Unit
$V_{CES}$	Collector-Emitter Voltage ( $V_{BE} = 0$ )	700	V
$V_{CEO}$	Collector-Emitter Voltage ( $I_B = 0$ )	400	V
$V_{EBO}$	Emitter-Base Voltage ( $I_C = 0$ )	9	V
$I_C$	Collector Current	4	A
$I_{CM}$	Collector Peak Current ( $t_p < 5$ ms)	8	A
$I_B$	Base Current	2	A
$I_{BM}$	Base Peak Current ( $t_p < 5$ ms)	4	A
$P_{tot}$	Total Dissipation at $T_c = 25$ °C	75	W
$T_{stg}$	Storage Temperature	-65 to 150	°C
$T_j$	Max. Operating Junction Temperature	150	°C



## ABSOLUTE MAXIMUM RATINGS

Symbol	Parameter	Value	Unit
$V_{CES}$	Collector-Emitter Voltage ( $V_{BE} = 0$ )	700	V
$V_{CEO}$	Collector-Emitter Voltage ( $I_B = 0$ )	400	V
$V_{EBO}$	Emitter-Base Voltage ( $I_C = 0$ )	9	V
$I_C$	Collector Current	4	A
$I_{CM}$	Collector Peak Current ( $t_p < 5$ ms)	8	A
$I_B$	Base Current	2	A
$I_{BM}$	Base Peak Current ( $t_p < 5$ ms)	4	A
$P_{tot}$	Total Dissipation at $T_c = 25$ °C	75	W
$T_{stg}$	Storage Temperature	-65 to 150	°C
$T_j$	Max. Operating Junction Temperature	150	°C

1. Control 24V? -> Yes

2. Can supply enough current? -> Yes.


- At 24V, the maximum current is  $75/24 = 3.125$  A
- 75W can be achieved only when  $T_c$  (case) is 25C.

# Higher loads



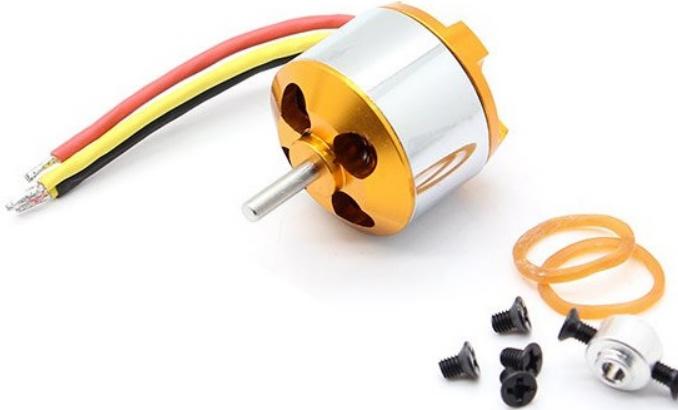**QR Y100**



The most easy control aircraft in the world



**Drone Motor  
14-25A**

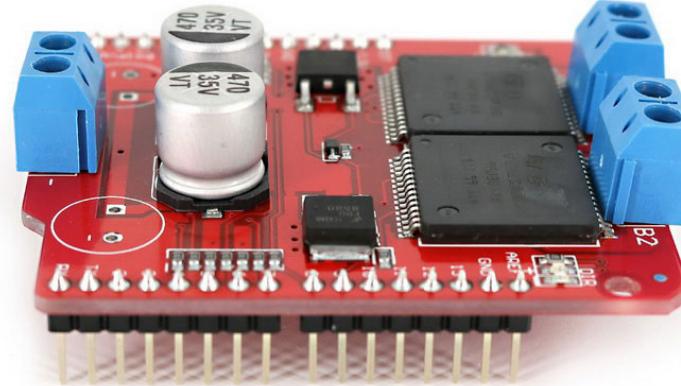
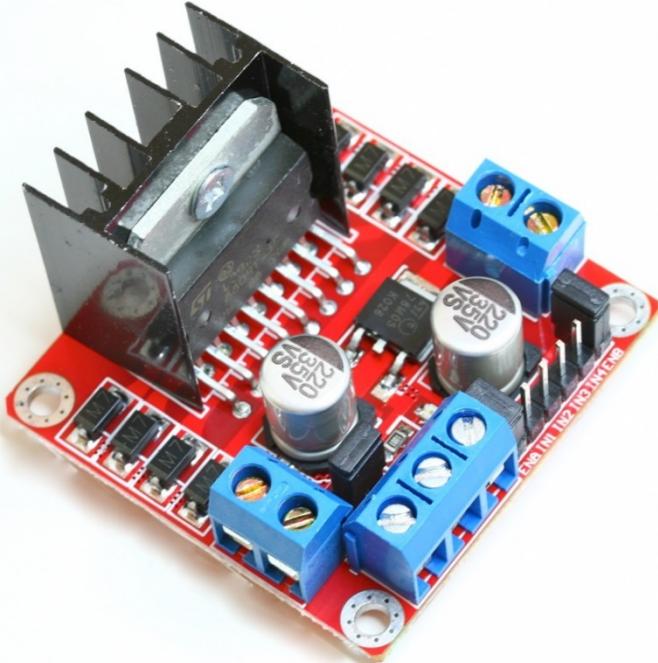
# Motor Driver Modules

Complex and more expensive but easy to use.



Current capacity 20-40 Amps typical


# Relays

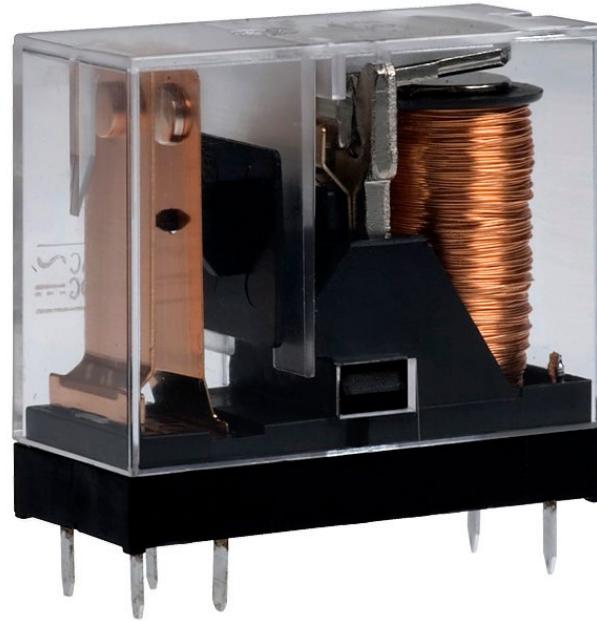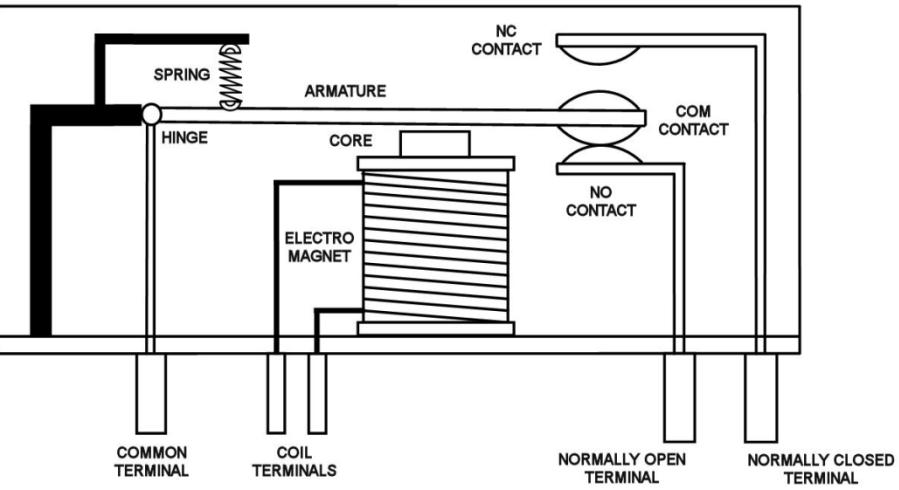



Usually have higher current ratings for its price.  
15-50 Amps @5V typical for less than 100 THB

# Relay “Poles” and “Throws”


SPST

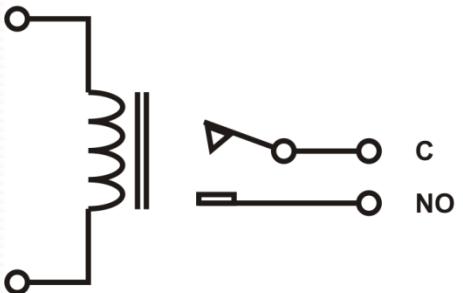

DPST

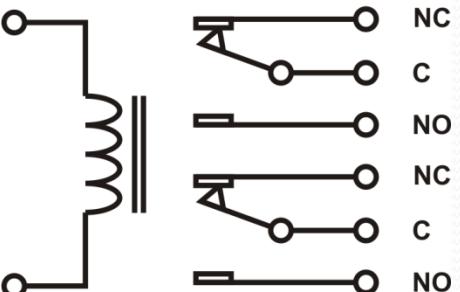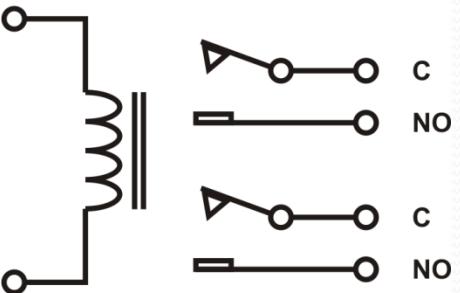

SPDT

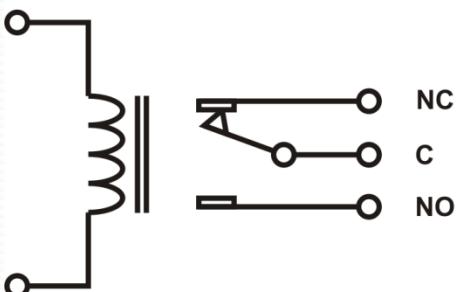



DPDT


Poles = How many circuits are there?  
Throws = Either NC or NO  
or both NC/NO

Note:  
NC = Normally Closed  
NO = Normally Opened


# Driving load with a relay

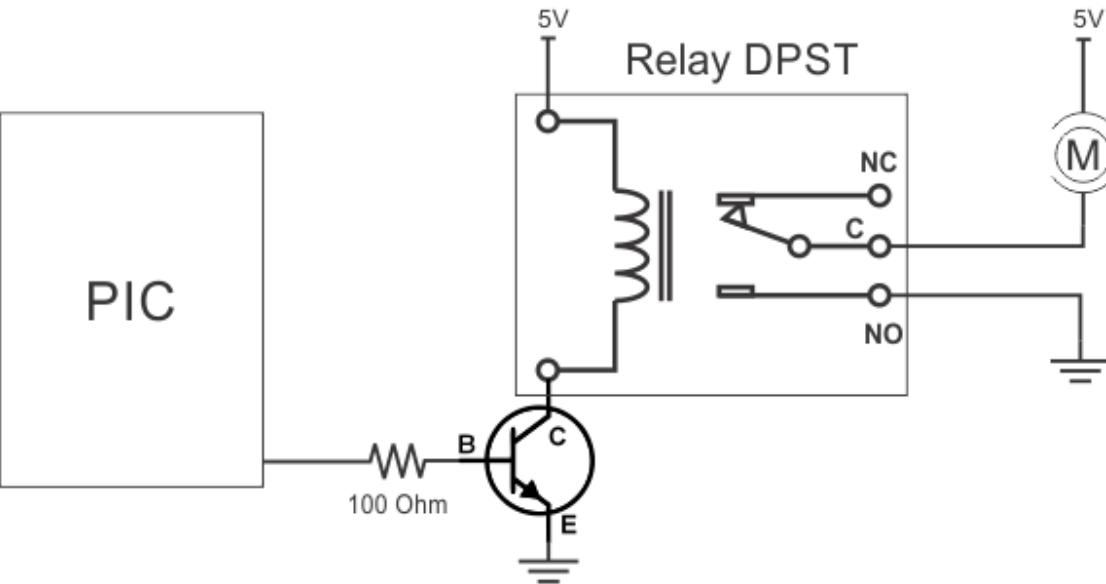

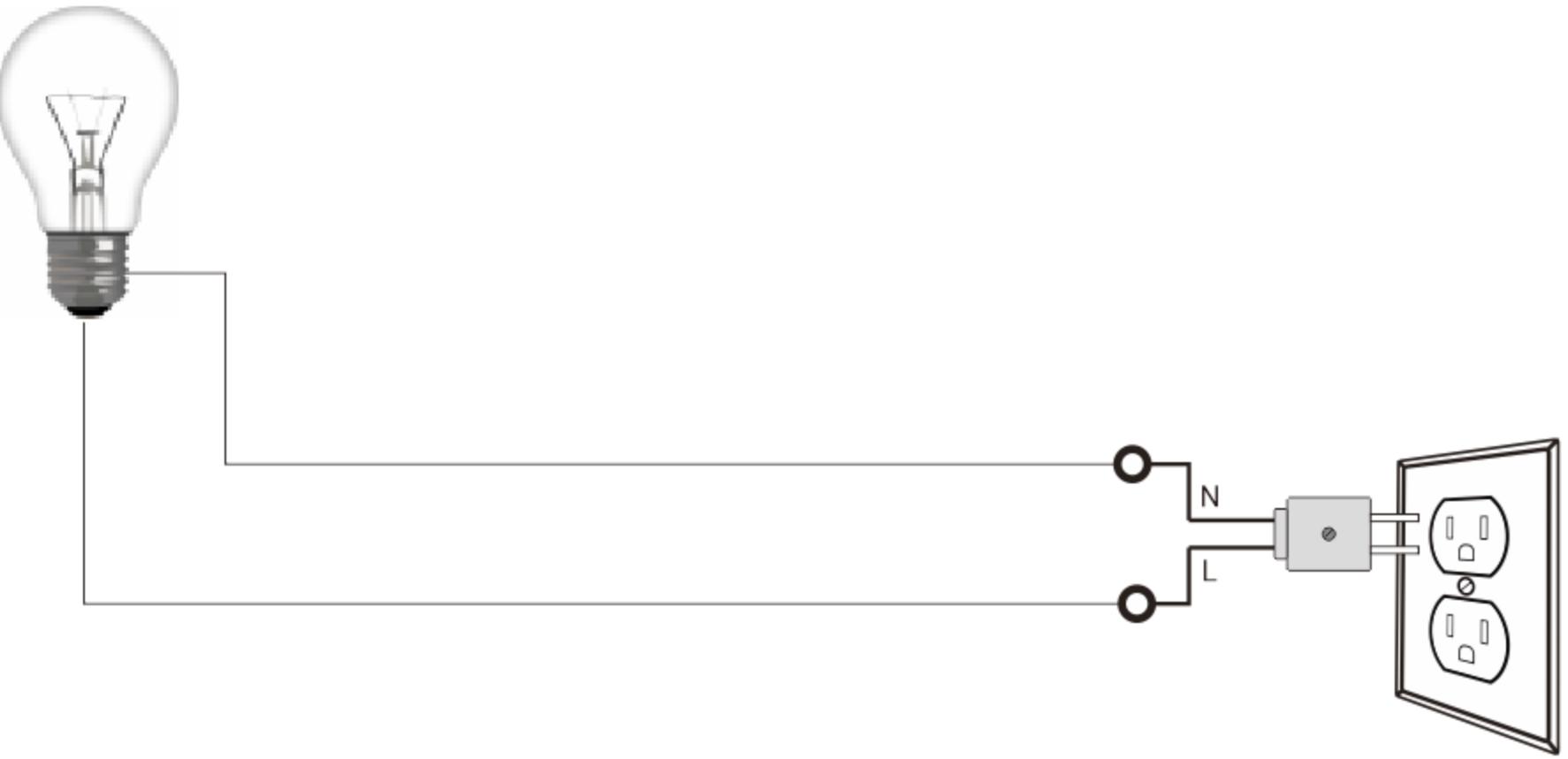



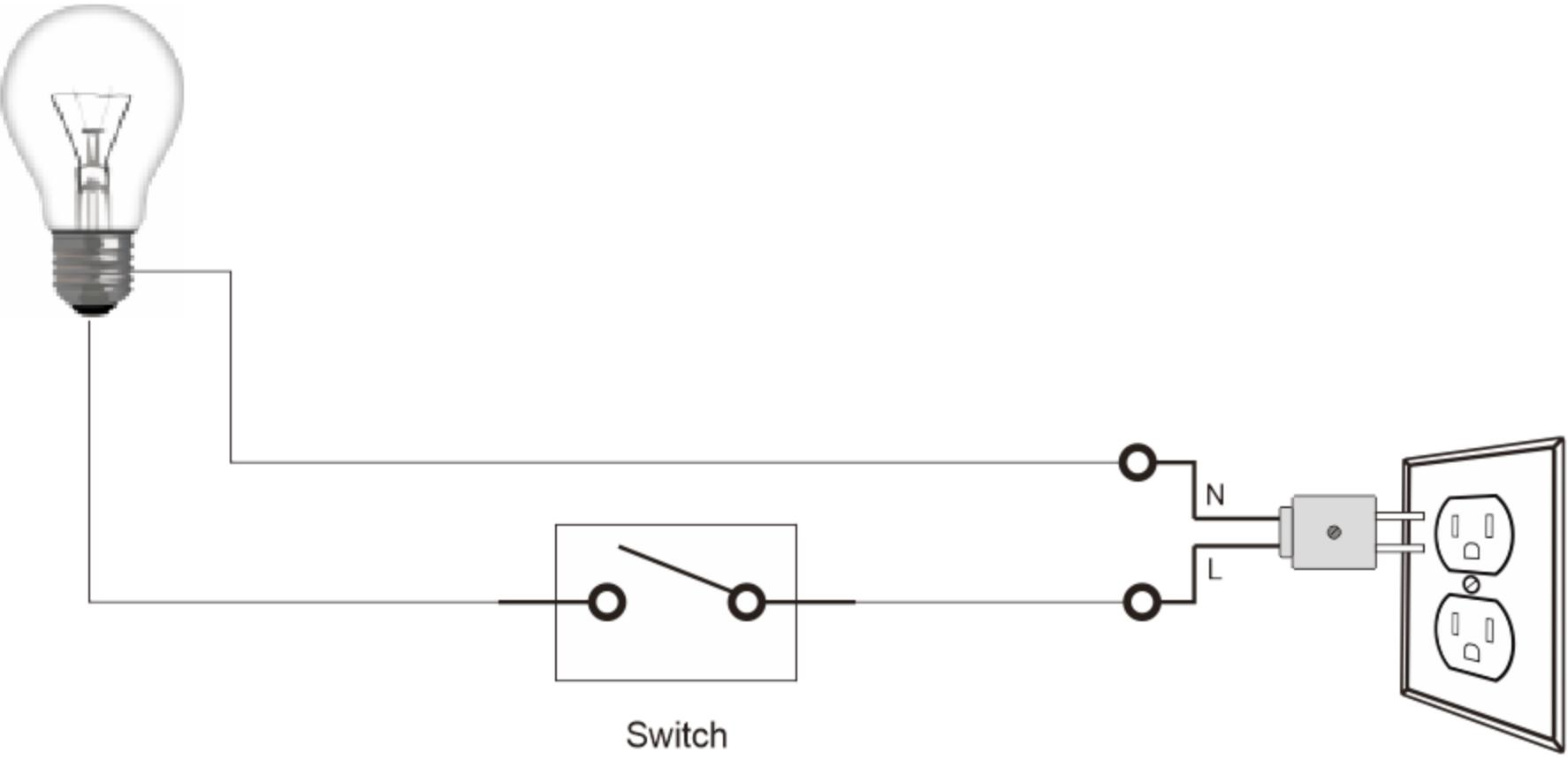


Switch


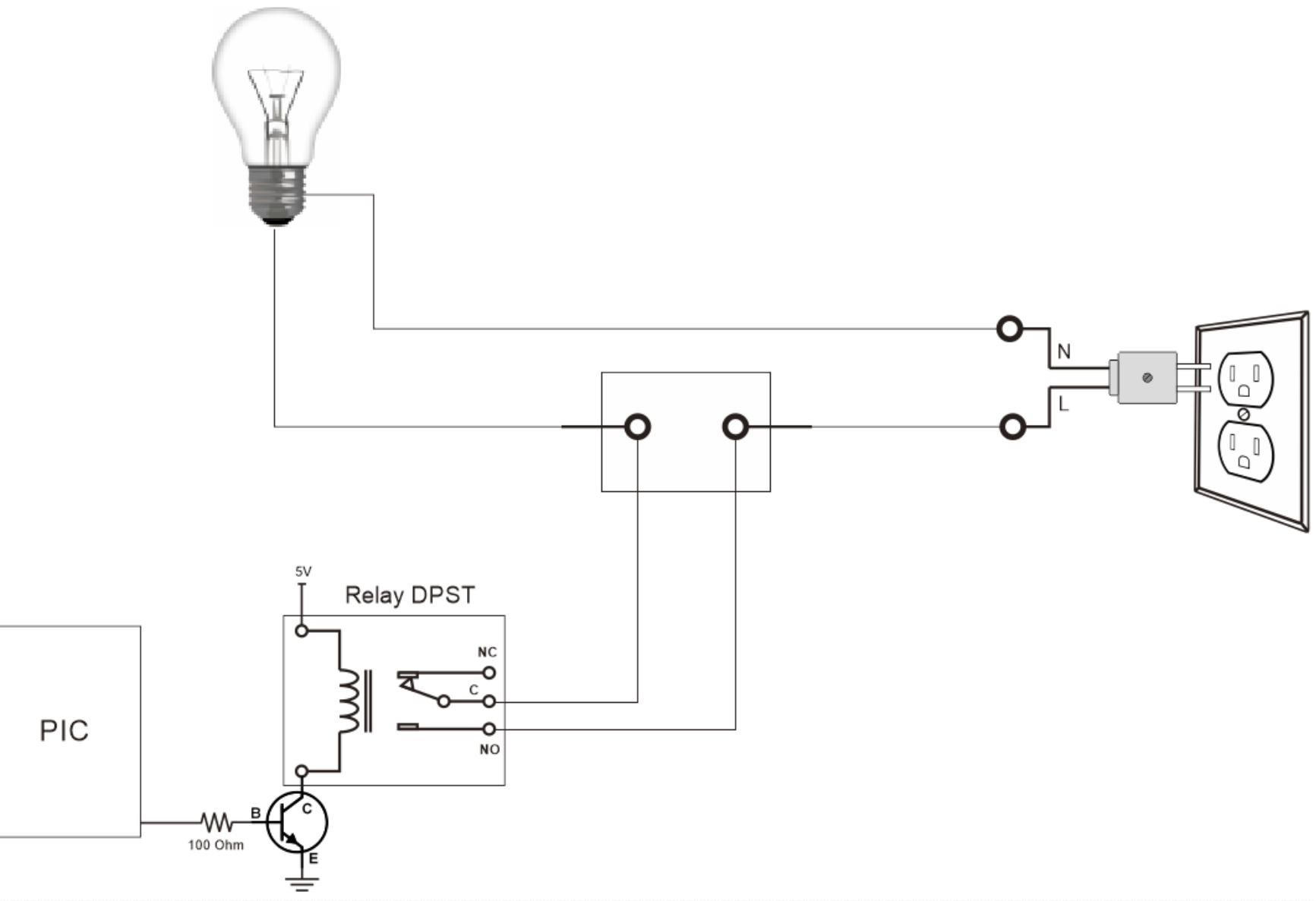


# H-Bridge: A bi-directional driver

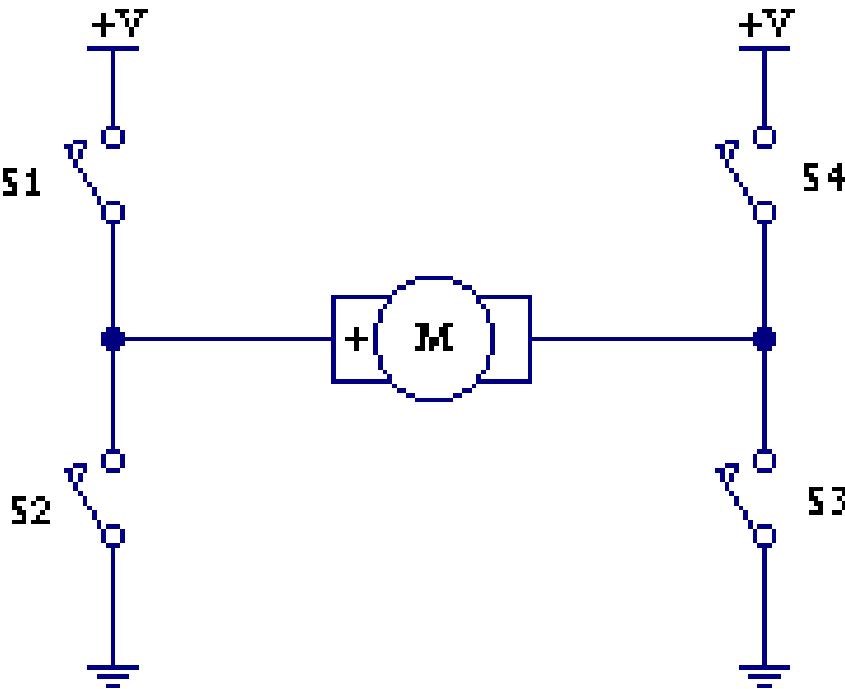


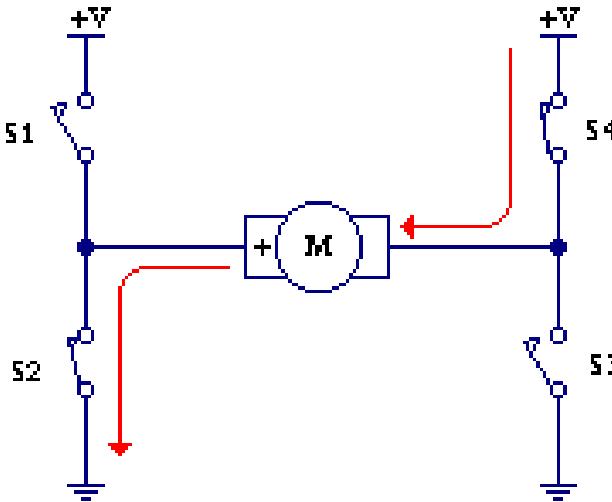
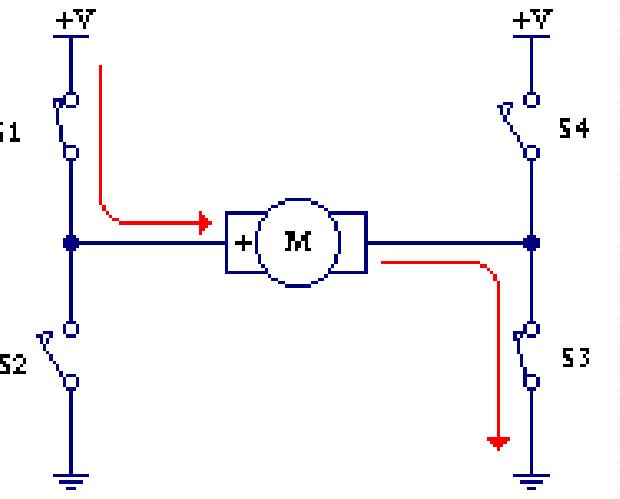


# Relay H-Bridge

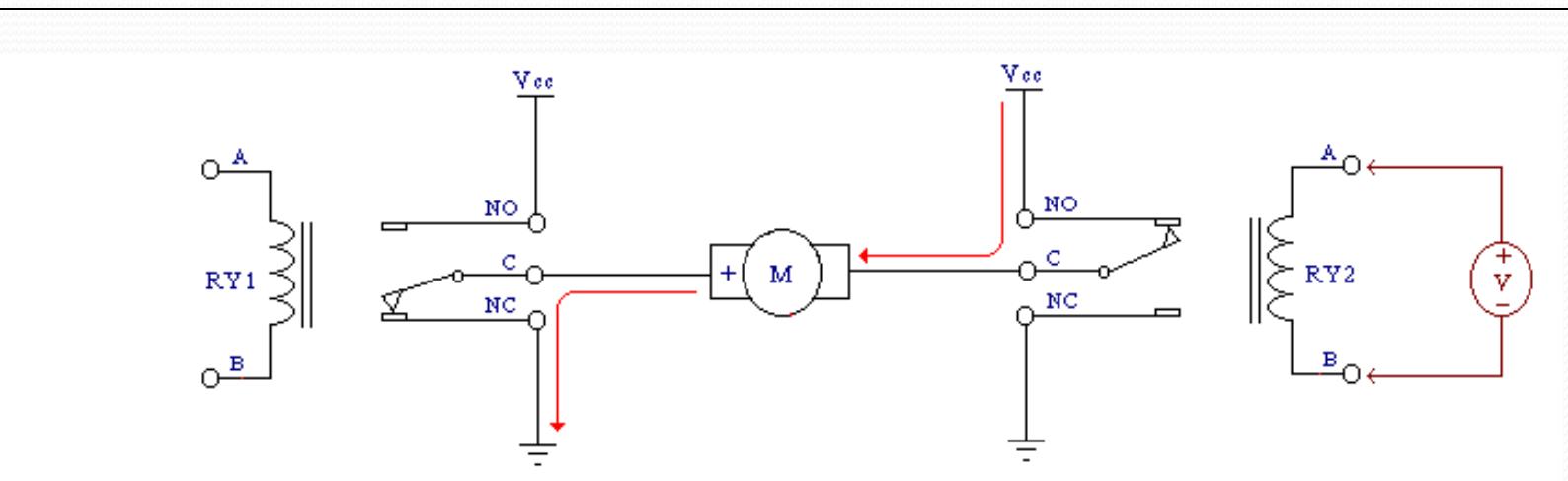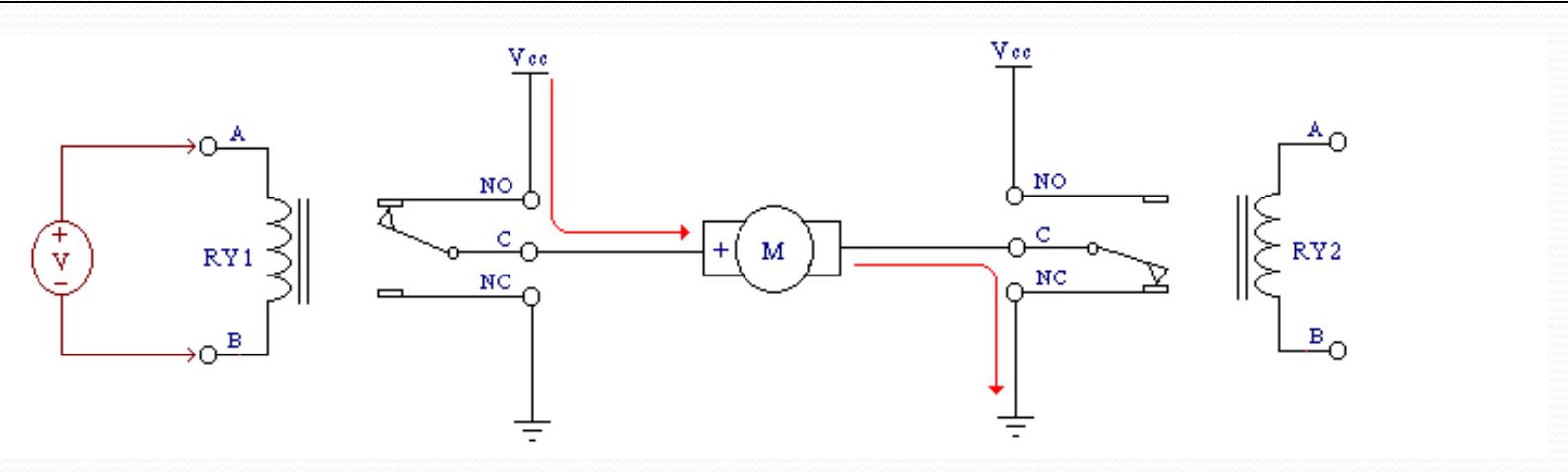

# Transistor H-Bridge

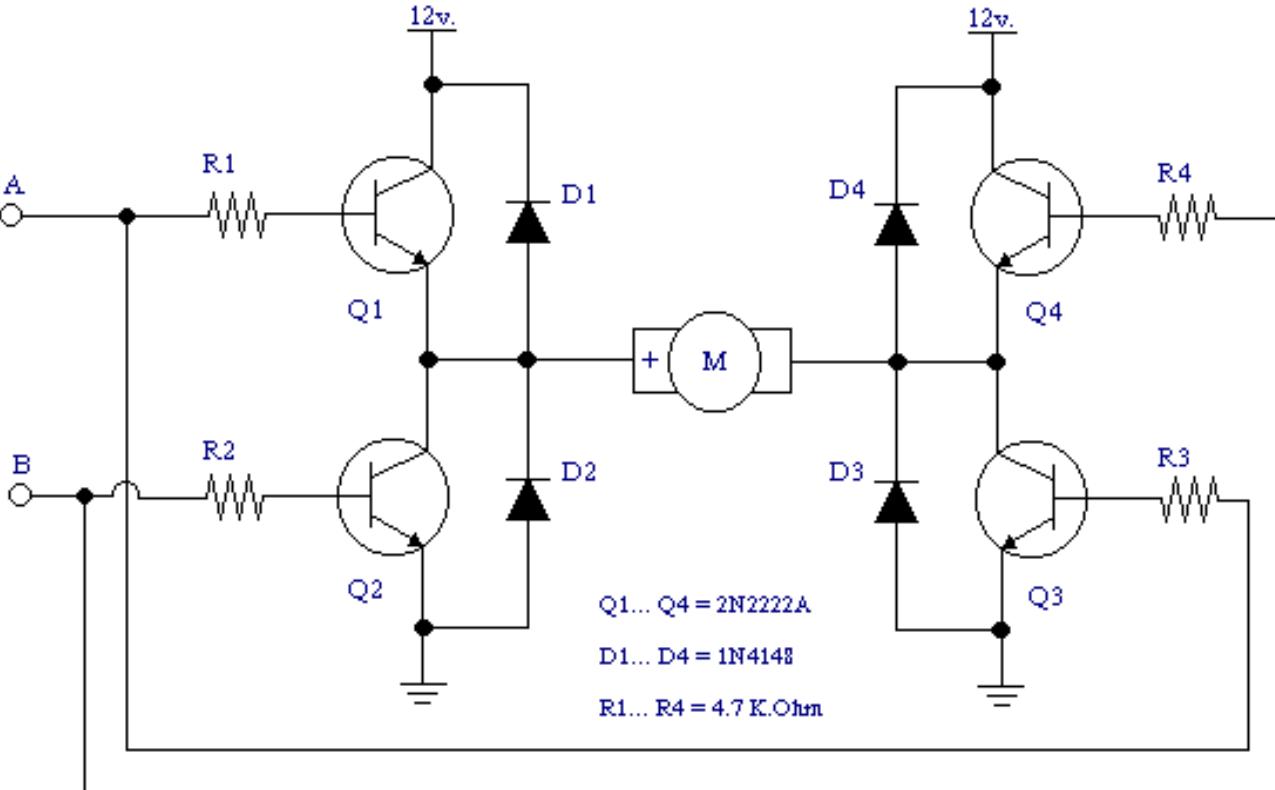


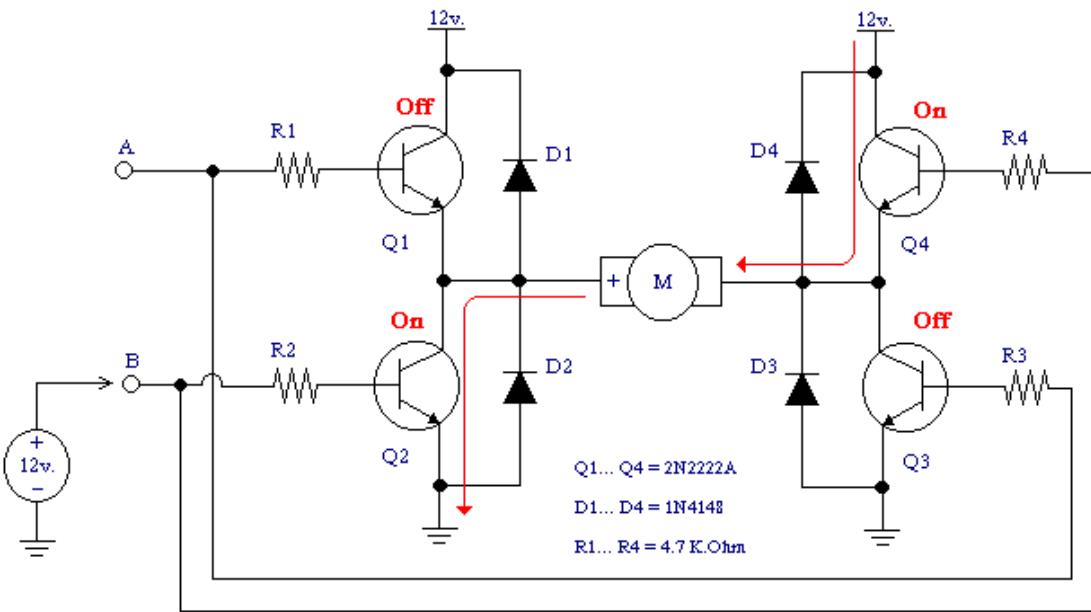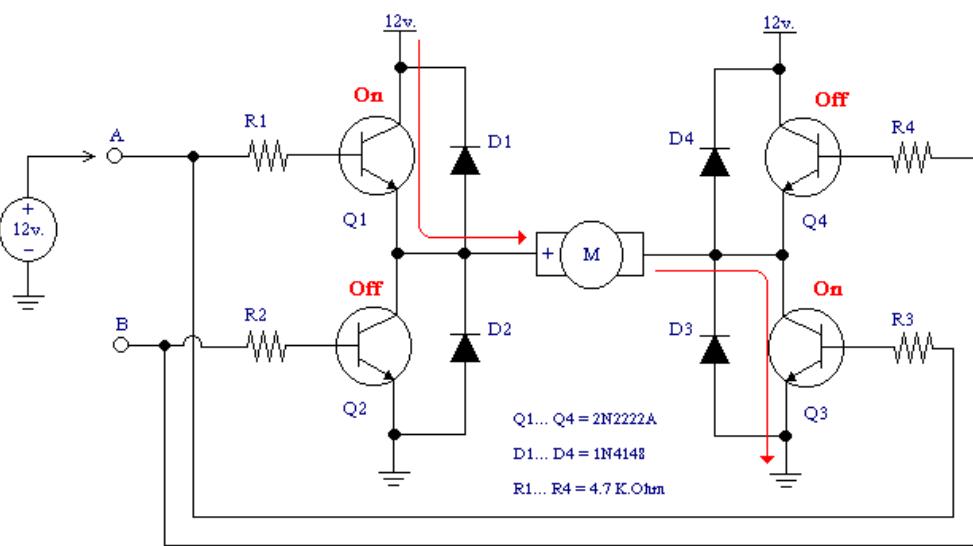

# Conclusions

- There are many ways to drive output devices
- Transistors are good for low power applications
- Relays are suitable for AC power applications or when low loss and high current is needed
- H-bridge is for bi-directional applications
- Choose the right tool for the job!

# 1. หลักการของ ADC

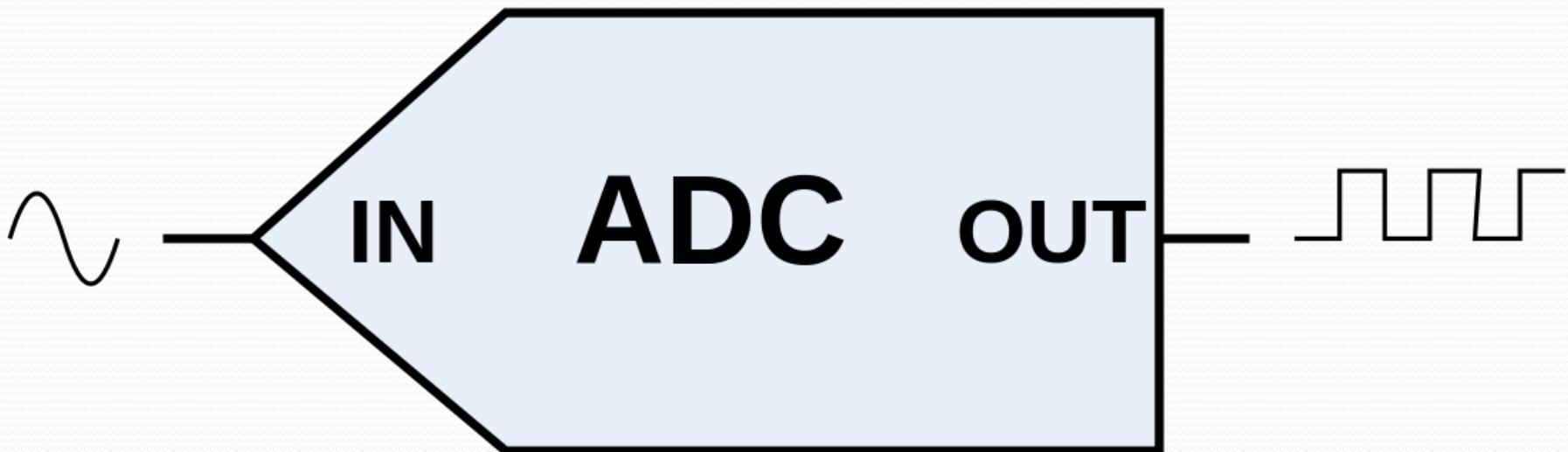


สัญญาณ

Analog (Voltage)

ค่า Digital
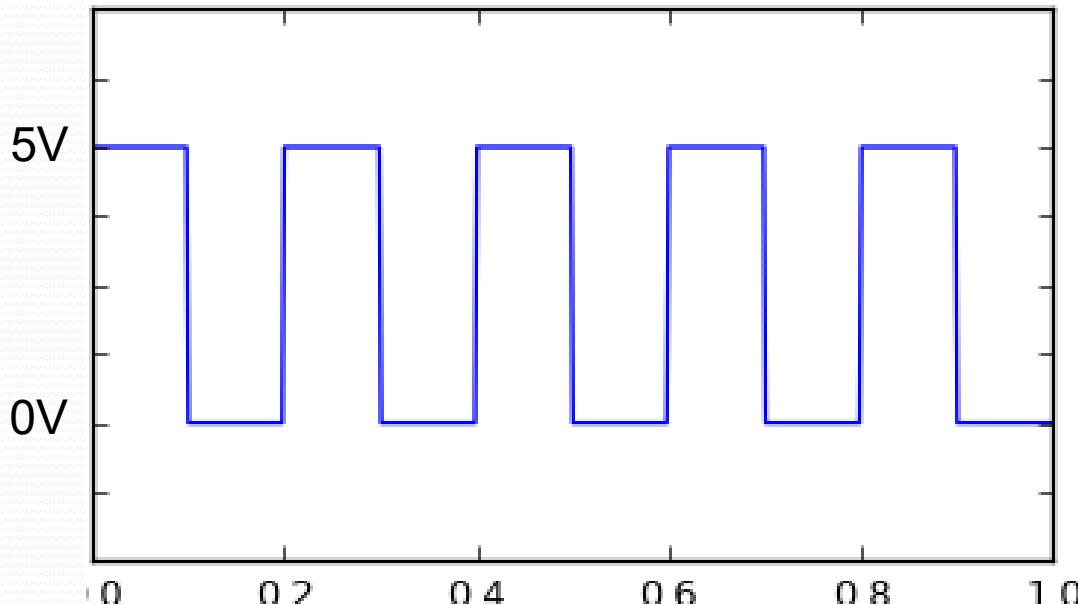
# 1.1 Sampling Rate Case Study: Speed Clicker Game

Player tries to press a button as many times as possible within a given time.




What is the minimum sampling rate in order to catch all the clicks?

$$\text{Pulse period} = 0.2 \text{ sec} \rightarrow \text{Freq} = 1/0.2 = 5 \text{ Hz}$$

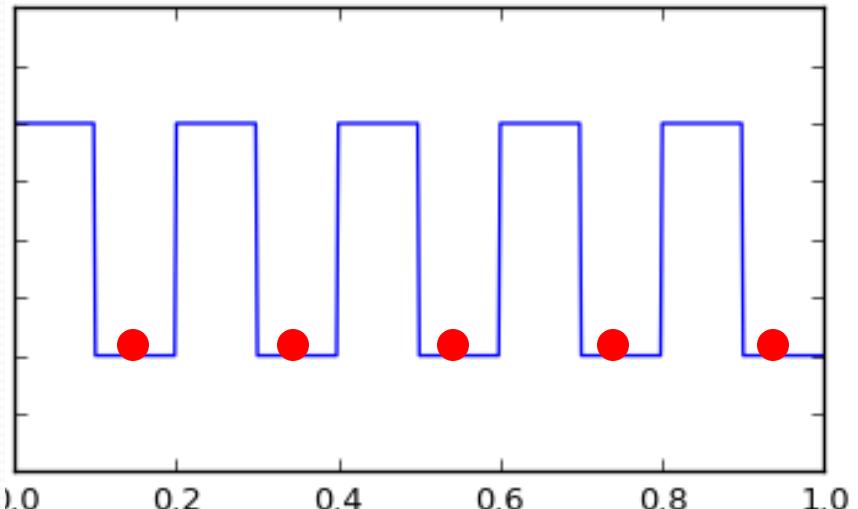
# Nyquist Frequency

Minimum sampling rate must be **2x the signal rate**.

- Slower sampling rates can cause “aliasing”




5Hz sampled output misses all the pulses

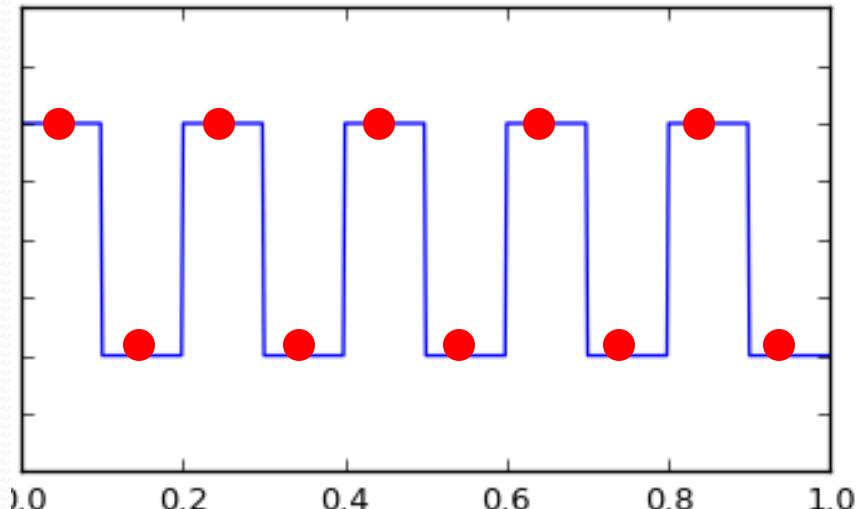

10Hz sampled output will capture the pulses

# 1.2 ADC Resolution

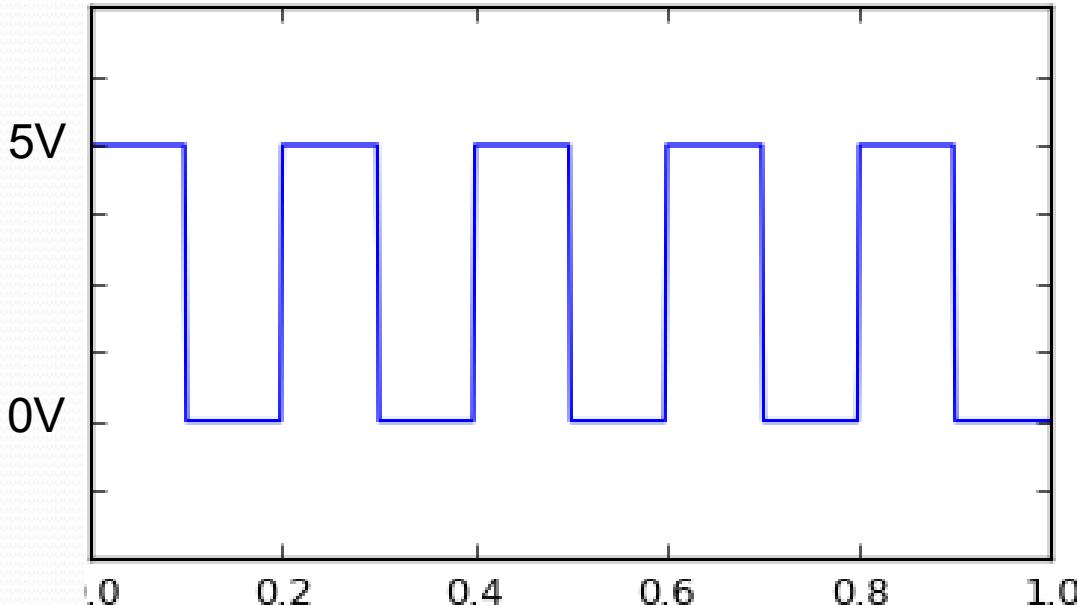

What is the minimum ADC resolution needed for this application

A Square wave has only two values: high and low  
Thus, a 1 bit ADC is sufficient

# How about the ESP32 mcu?



## 4.1.2 Analog-to-Digital Converter (ADC)

ESP32 integrates 12-bit SAR ADCs and supports measurements on 18 channels (analog-enabled pins).

Table 7 describes the ADC characteristics.

**Table 7: ADC Characteristics**

Parameter	Description	Min	Max	Unit
DNL (Differential nonlinearity)	RTC controller; ADC connected to an external 100 nF capacitor;	-7	7	LSB
INL (Integral nonlinearity)	DC signal input; ambient temperature at 25 °C; Wi-Fi&BT off	-12	12	LSB
Sampling rate	RTC controller	-	200	ksps
	DIG controller	-	2	Msps

Sampling rate is very good.  
But the ADC resolution is not very high for audio.

# High-end Sound Card

Sound BlasterX AE-5



\$140.00

BUY

The Sound BlasterX AE-5 is a SABRE<sup>32</sup> Ultra Class PCIe DAC which is perfect for hi-resolution audio for games, music, and movies. It delivers up to 32-bit 384kHz playback with a 122dB DNR, ultra-low distortion and jitter.

**32bit**  
**384kHz**

**DISCRETE**  
**5.1**  
SURROUND

**VIRTUAL**  
**7.1**  
SURROUND

**122**  
dB  
DAC




### 3. Number of ADC ports


Device	Program Memory		Data Memory		I/O	10-bit A/D (ch)	ECCP/ CCP	EUSART	MSSP	Comparators	Timers 8/16-bit
	Flash (words)	SRAM (bytes)	EEPROM (bytes)								
PIC16F882	2048	128	128	24	11	1/1	1	1	2	2/1	
PIC16F883	4096	256	256	24	11	1/1	1	1	2	2/1	
PIC16F884	4096	256	256	35	14	1/1	1	1	2	2/1	
PIC16F886	8192	368	256	24	11	1/1	1	1	2	2/1	
PIC16F887	8192	368	256	35	14	1/1	1	1	2	2/1	

# Which pins are ADC pins?

Not all pins are analog-capable

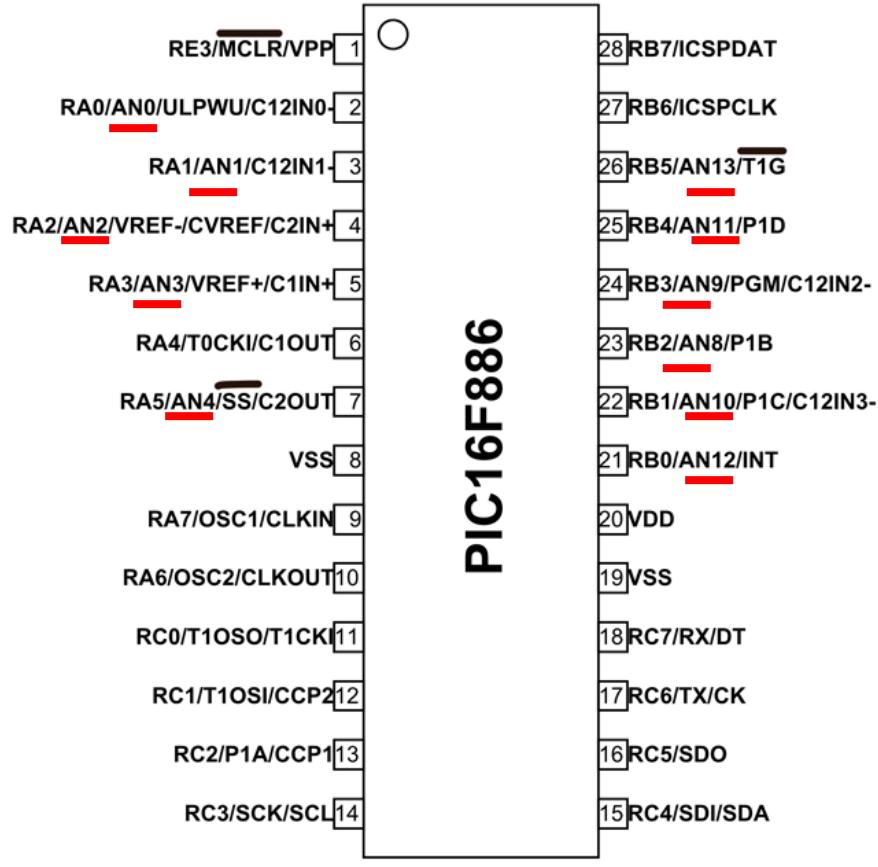

## ESP32 PINOUT

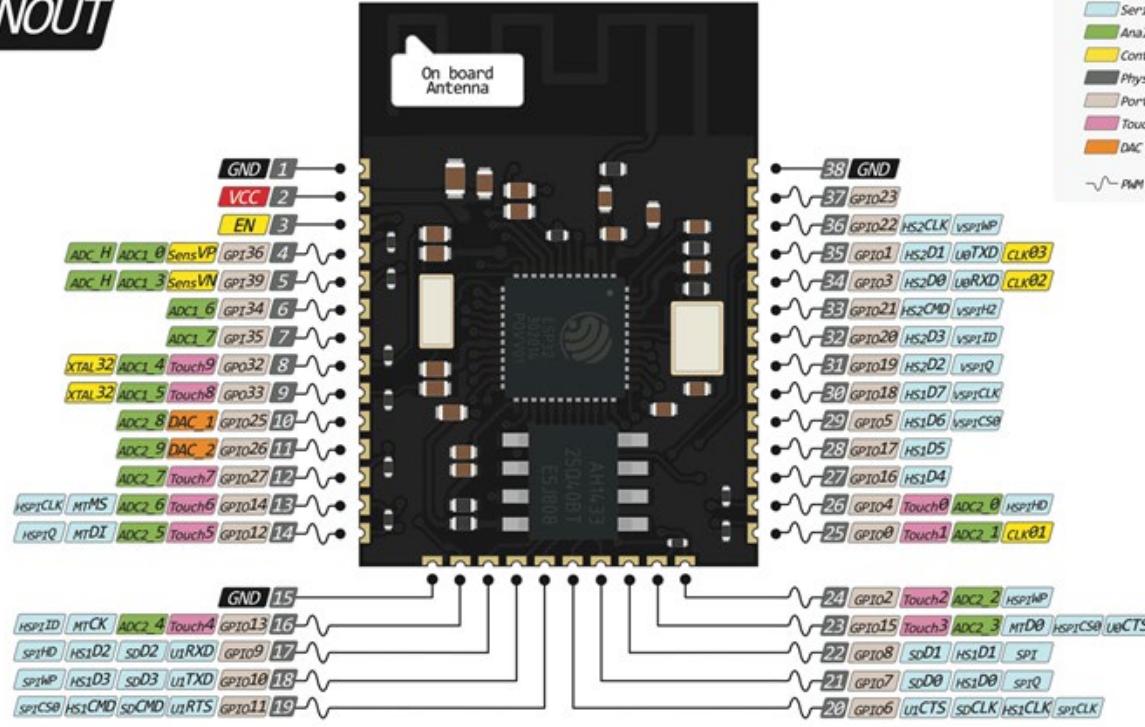


<http://esp32.com/>

Power  
GND  
Serial Pin  
Analog Pin  
Control  
Physical Pin  
Port Pin  
Touch Pin  
DAC Pin  
PWM Pin
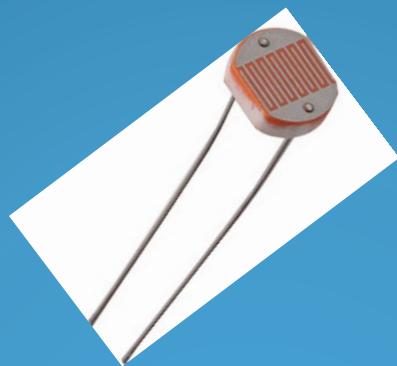
## 2. วงจรแบ่งแรงดัน (Voltage Divider)

บ่อยครั้งที่ sensor เป็นตัวต้านทาน แต่ ADC วัดได้แค่แรงดันไฟฟ้า  
เราจะเปลี่ยนความต้านทานให้เป็นแรงดันได้อย่างไร



# ตัวอย่างวงจรแบ่งแรงดัน


V เข้า MCU แปรผัน

ตามค่า R ของเซ็นเซอร์

AN0 RA0	2
AN1 RA1	3
AN2 RA2	4
AN3 RA3	5
RA4	6
AN4 RA5	7
RA6	10



# Voltage Divider Circuit

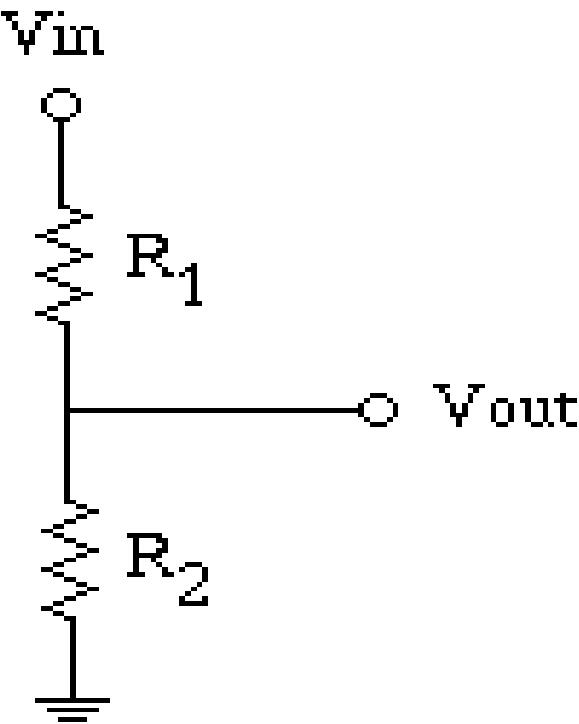


$$V_{out} = \frac{R_2}{R_1 + R_2} \cdot V_{in}$$

และเนื่องจาก  $ADC\ Output \propto V_{out}$

$$\therefore ADC\ Output = \frac{R_2}{R_1 + R_2} \cdot Max\ ADC\ Value$$

## ตัวอย่างการคำนวณ

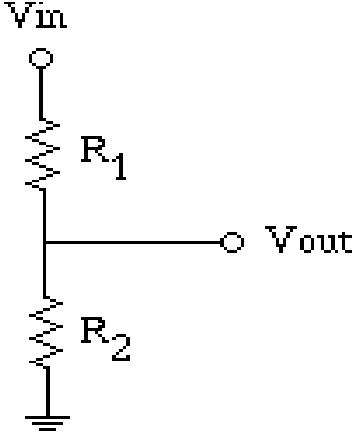

ถ้า  $R_2 = 33K$ ,  $V_{in} = 5V$

ถ้า  $R_{sensor} (R_1) = 99K$


- ค่าที่อ่านจาก ADC จะเป็นเท่าใด? (1.25V)
- ค่า ADC Output จะเป็นเท่าใด? (255 ถ้าใช้ ADC 10 bit)
- ถ้าสลับตำแหน่ง  $R_{sensor}$  กับ  $R$  อ้างอิงคำตอบข้างต้นจะเปลี่ยนแปลงไปอย่างไร

### 3. ADC Conversion Methods

(เนื้อหาเสริม)


- Direct conversion (Flash ADC)
- Ramp-compare ADC
- Successive-Approximation

# 1. Direct Conversion

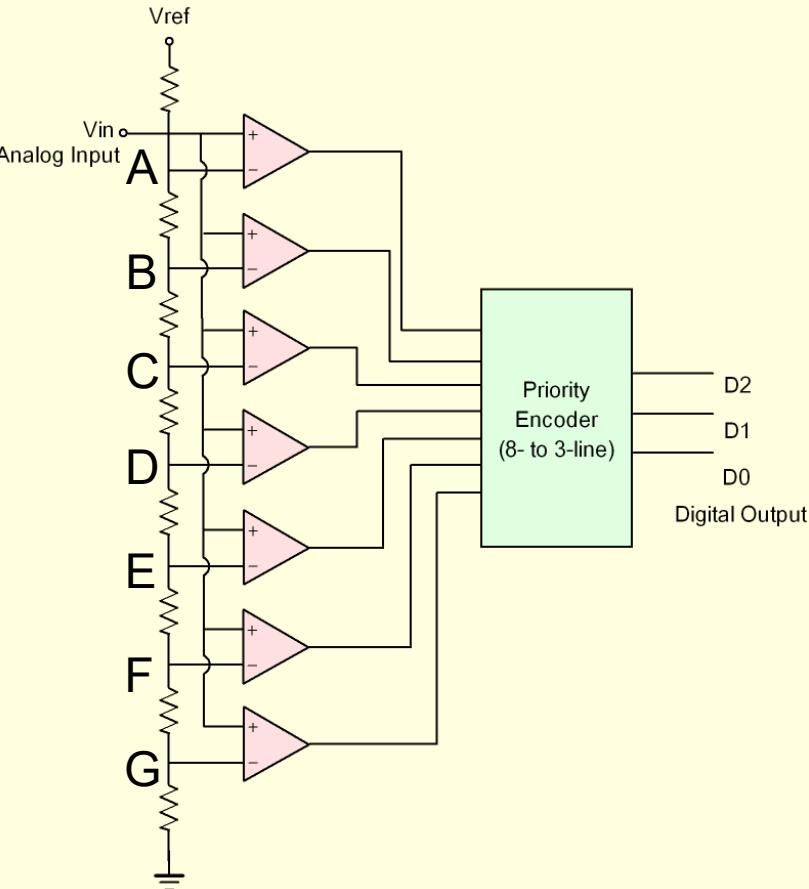


แรงดันอ้างอิง ( $V_{ref}$ ) จะถูกแบ่งค่าลงเรื่อยๆ และป้อนเข้าชุดวงจรเปรียบเทียบแรงดัน วงจรเปรียบเทียบได้ที่  $V_{in}$  มากกว่า  $V_{ref}$  ก็จะให้ค่าเป็น 1 วงจรที่เหลือจะให้ค่าเป็น 0

# OpAmp as a Comparator

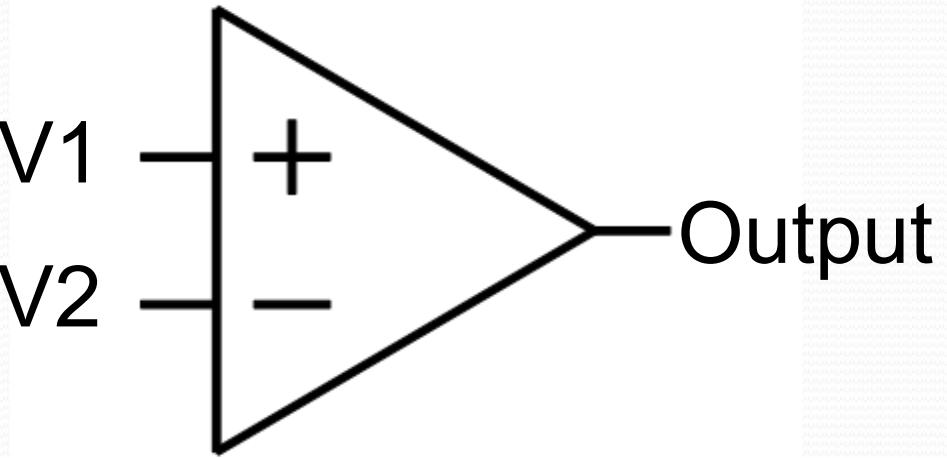


Input	Output
$V_1 > V_2$	High (1)
$V_1 < V_2$	Low (0)

# Voltage Divider

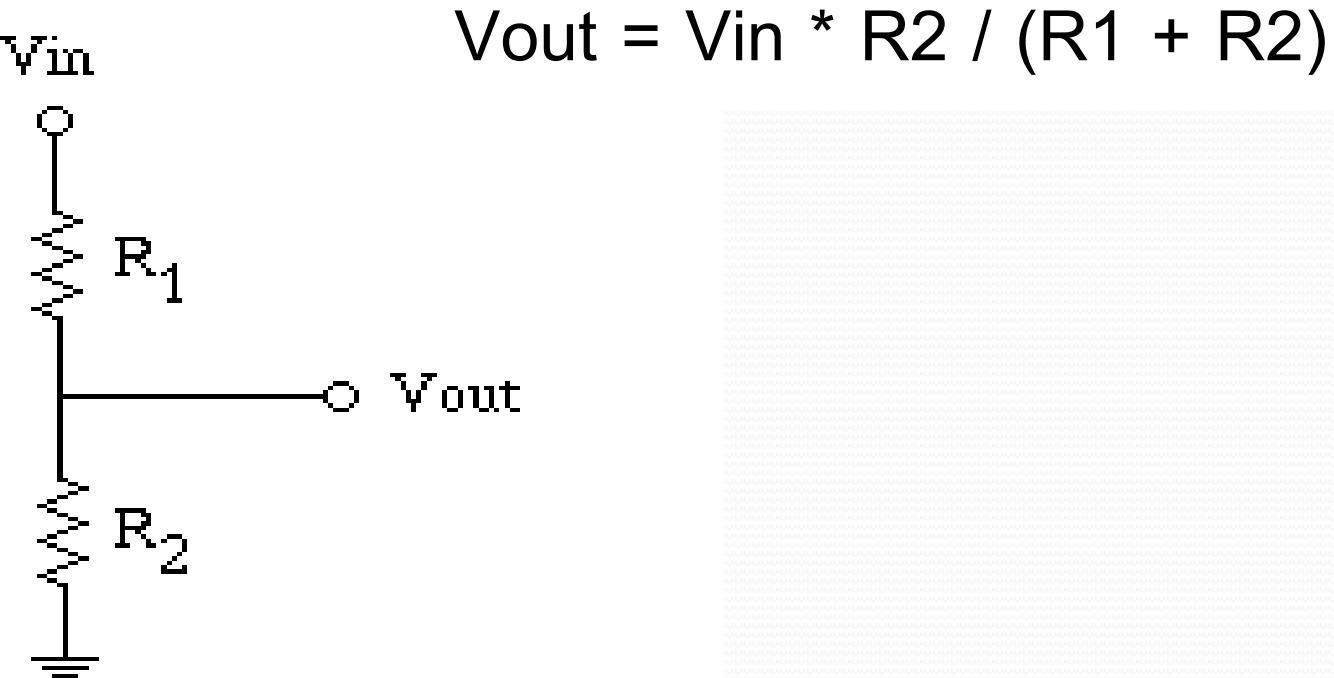

# Direct Conversion

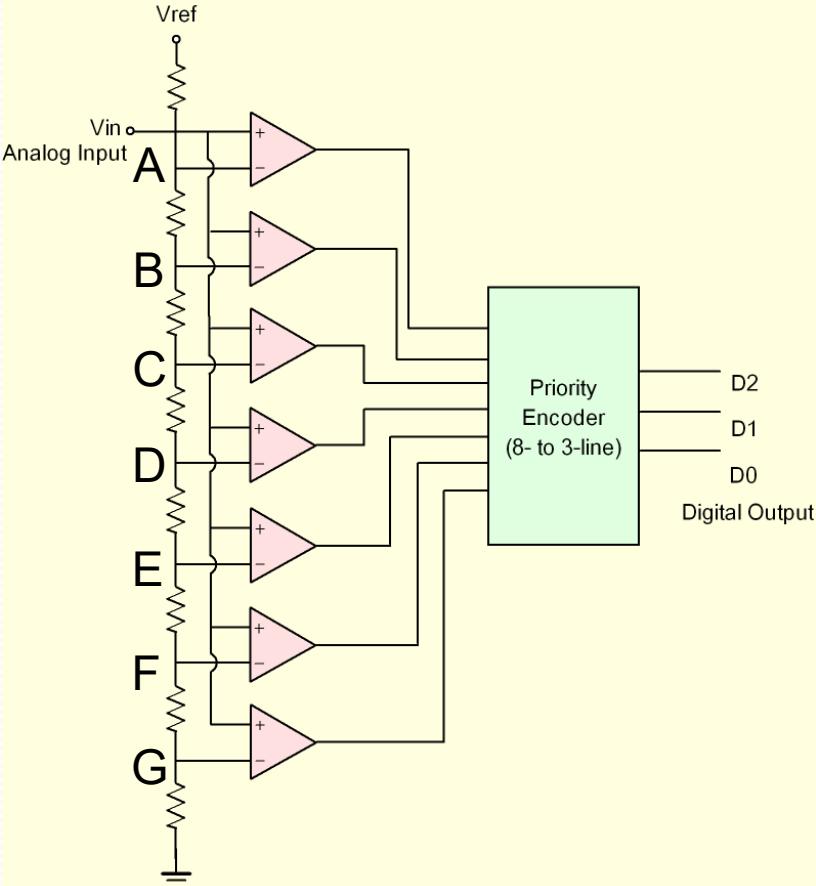

$$V \text{ at } A = V_{ref} * 7R / 8R$$

$$V \text{ at } B = V_{ref} * 6R / 8R$$

...

$$V \text{ at } G = V_{ref} * R / 8R$$


$$V \text{ at } A = V_{ref} * 7/8$$

$$V \text{ at } B = V_{ref} * 6/8$$

...

$$V \text{ at } G = V_{ref} * 1/8$$

# Direct Conversion

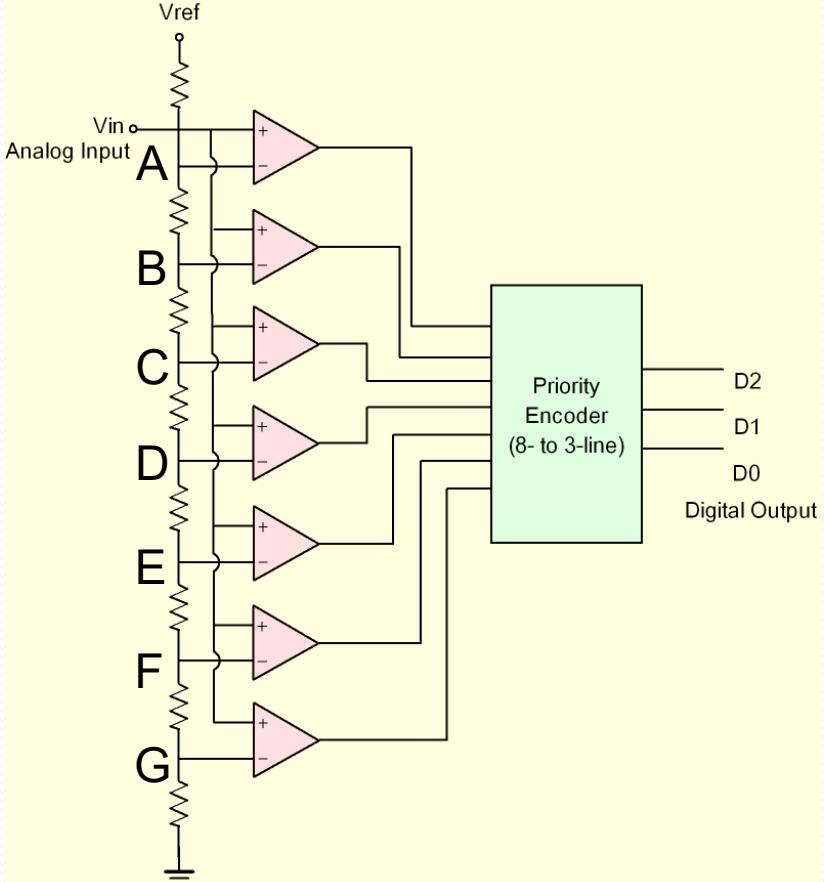


If  $V_{ref} = 8V$  and  $V_{in} = 5.5 V$   
What is the output of the ADC?

Output of comparator = 0b0011111  
Output of encoder = 0b101

**Demo**


## 2. Ramp-Compare ADC

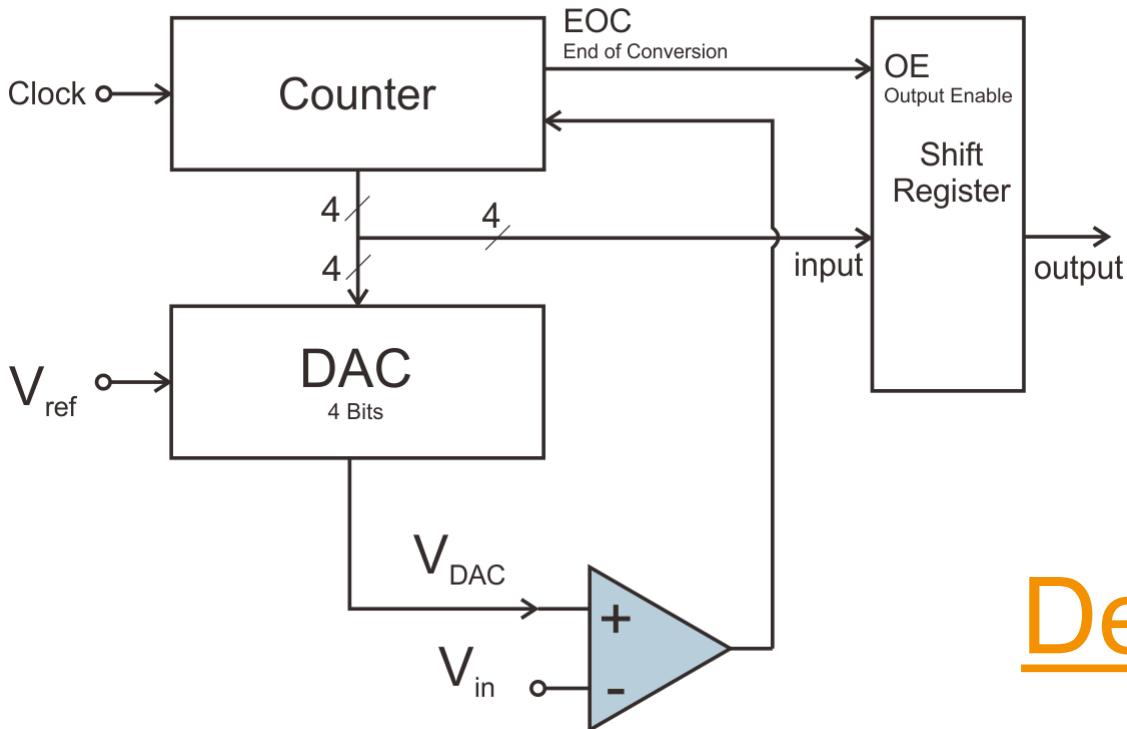

Demo


ใช้วงจรเปรียบเทียบแรงดันเพียงชุดเดียว โดยมีวงจรสร้างดัน (DAC) ค่อยๆ เพิ่มแรงดัน  
เปรียบเทียบขึ้นจนมีค่าเกิน  $V_{in}$

# Ramp-Compare ADC Signal Example

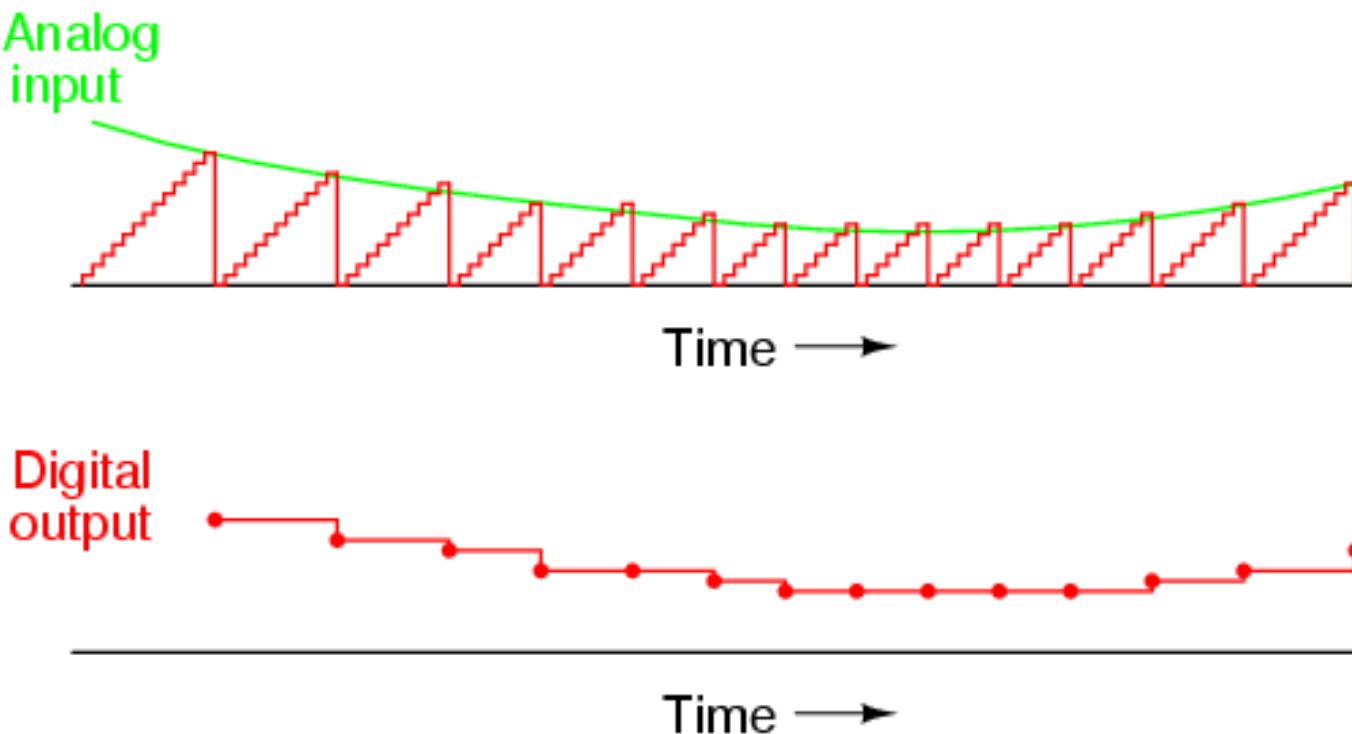

ข้อเสียอย่างหนึ่งของ Ramp-Compare คือใช้เวลาในการแปลงค่าไม่เท่ากัน Analog Input ที่มีค่ามากจะใช้เวลาแปลงนานกว่า ซึ่งเวลาที่แตกต่างกันนี้อาจส่งผลต่อจังหวะการทำงานของ MCU

### 3. Successive-Approximation

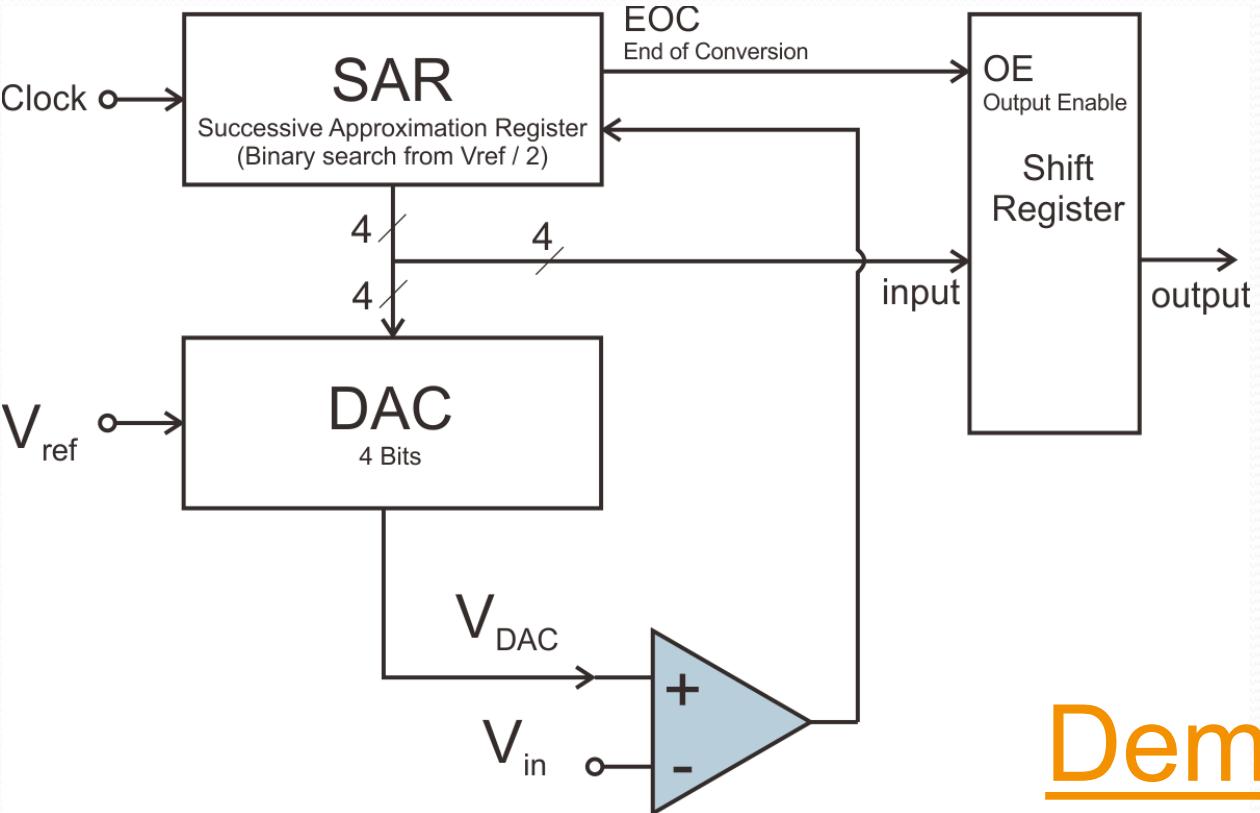

Demo

คือ Ramp Compare ADC ที่ปรับปรุงโดยใช้หลักของ Binary Search ในการหาค่าที่ใกล้เคียง  $V_{in}$  ที่สุด (แทนการค่อยๆ เพิ่มค่าจากน้อยไปมาก)

# ปัญหาของการใช้ threshold ค่าเดียวในการควบคุม

---

```
while(true) {  
    If sensor1 < 500 [ turnOn(); ]  
    If sensor1 > 500 [ turnOff(); ]  
}
```

# ปัญหาของการใช้ threshold ค่าเดียวในการควบคุม (ต่อ)

---

- ✖ ค่าเซ็นเซอร์จำนวนมากมีการแกว่ง
- ✖ บางครั้งเกิด Feedback จาก output เช่น
  - + ปั๊มน้ำอัตโนมัติ: ลูกloy ไม่อยู่นิ่ง เพราะน้ำกระเพื่อมจากน้ำที่ปั๊มสูบเข้า
  - + โคมไฟอัตโนมัติ: แสงจากหลอดไฟบางส่วนตกกลับไปตอกกระหบเซ็นเซอร์แสง

# การติดดับติดต่อกันมักส่งผลเสียต่ออุปกรณ์

---


- ✖ เกิดไฟกระชากบ่อยครั้งหากเป็นอุปกรณ์ที่กินพลังงานมาก เช่น ปั๊มน้ำ รีเลย์
- ✖ อายุการใช้งานของอุปกรณ์สั้นลง
- ✖ ส่งผลให้ผู้ใช้เกิดความรำคาญ กระทบต่อการใช้งานจริง [[ตัวอย่าง 7-Eleven](#)]

# การใช้ Hysteresis แก้ไขปัญหา

---

กำหนด on threshold และ off threshold แยกกัน

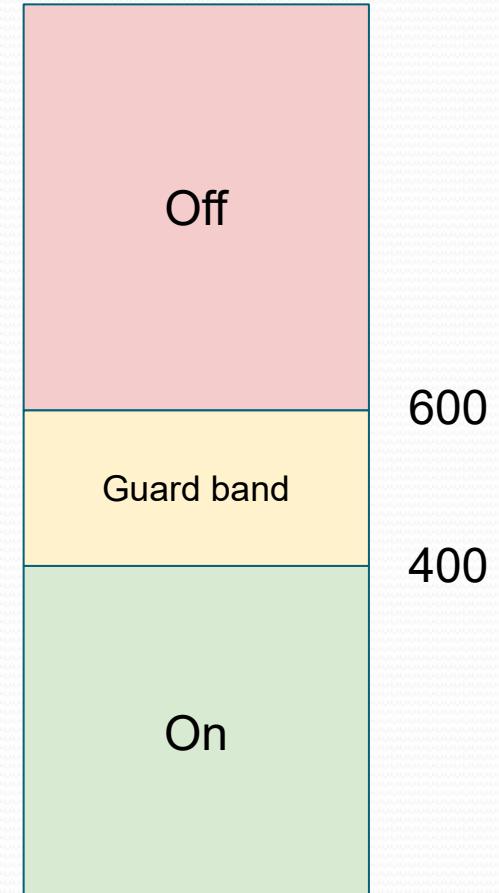
```
while(true) {  
    If sensor1 < 400 [ turnOn(); ]  
    If sensor1 > 600 [ turnOff(); ]  
}
```



# บางครั้งเซ็นเซอร์มี hysteresis ในตัว





ลูกloyไฟฟ้า

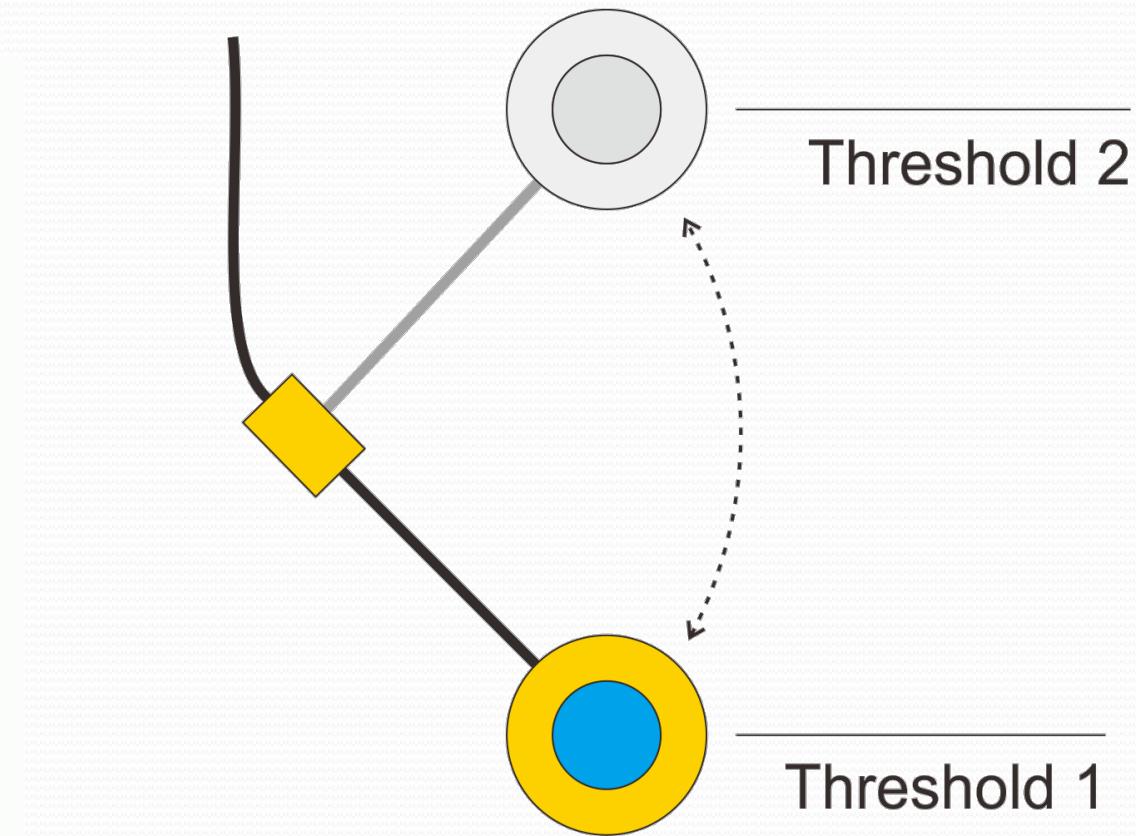


สวิตด้านในจะสับและปล่อยที่ระดับต่างกัน

# Typical Use: Water Pump Control

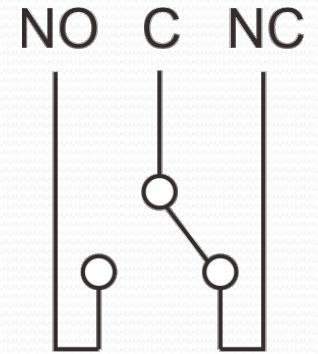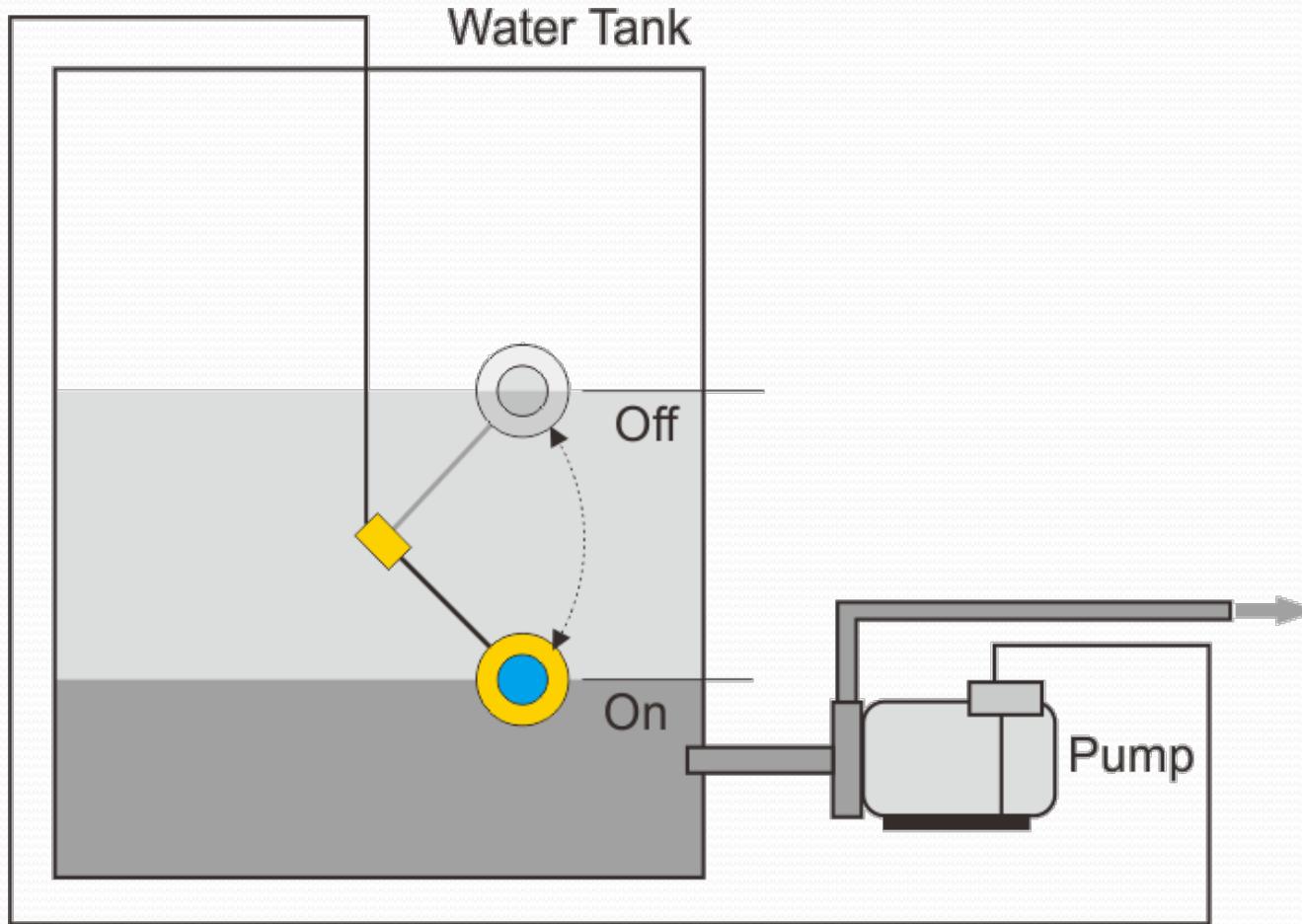


Sensor Pinout
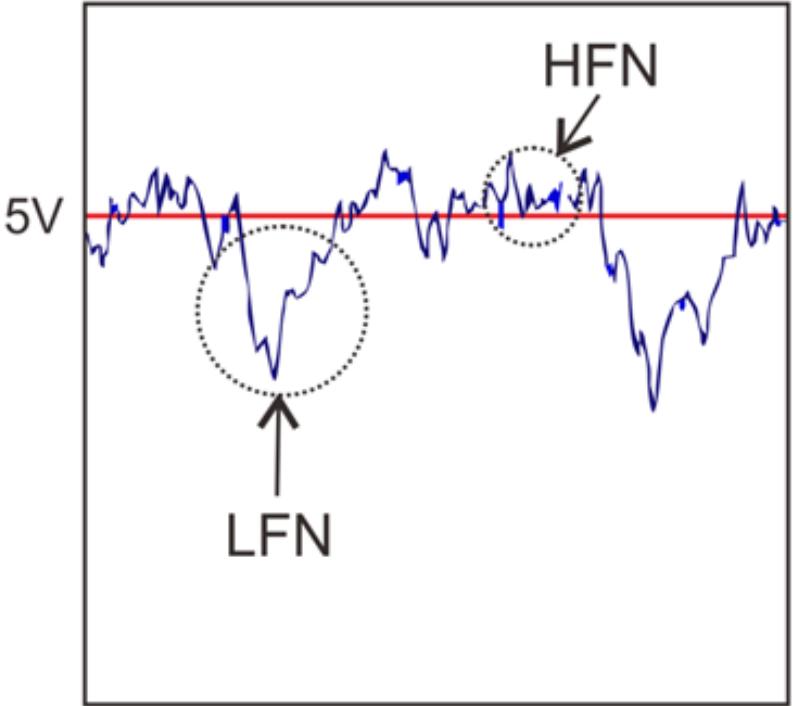
# Simple Low-Pass Filtering: Hardware Filtering using Capacitors




No Capacitor

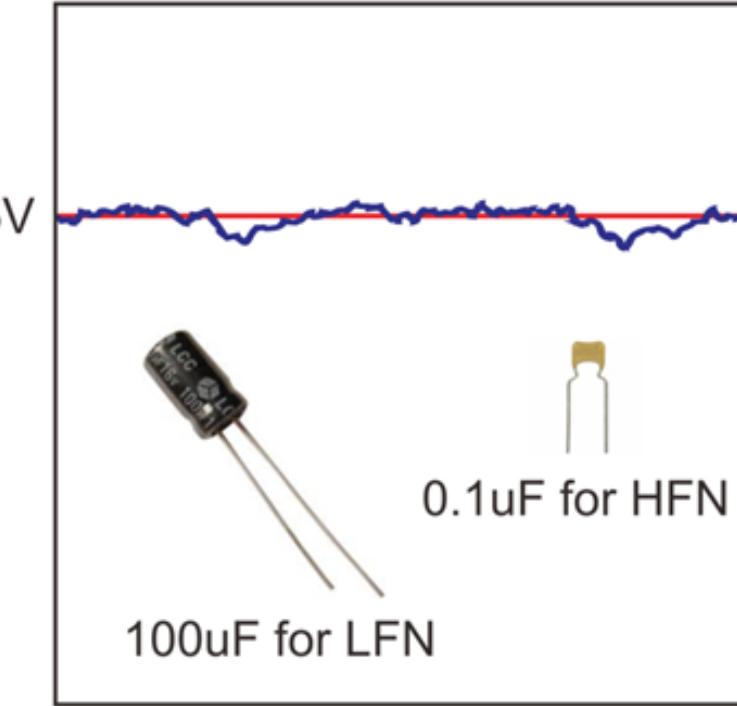



With Capacitor

# Capacitors slow down the signal change

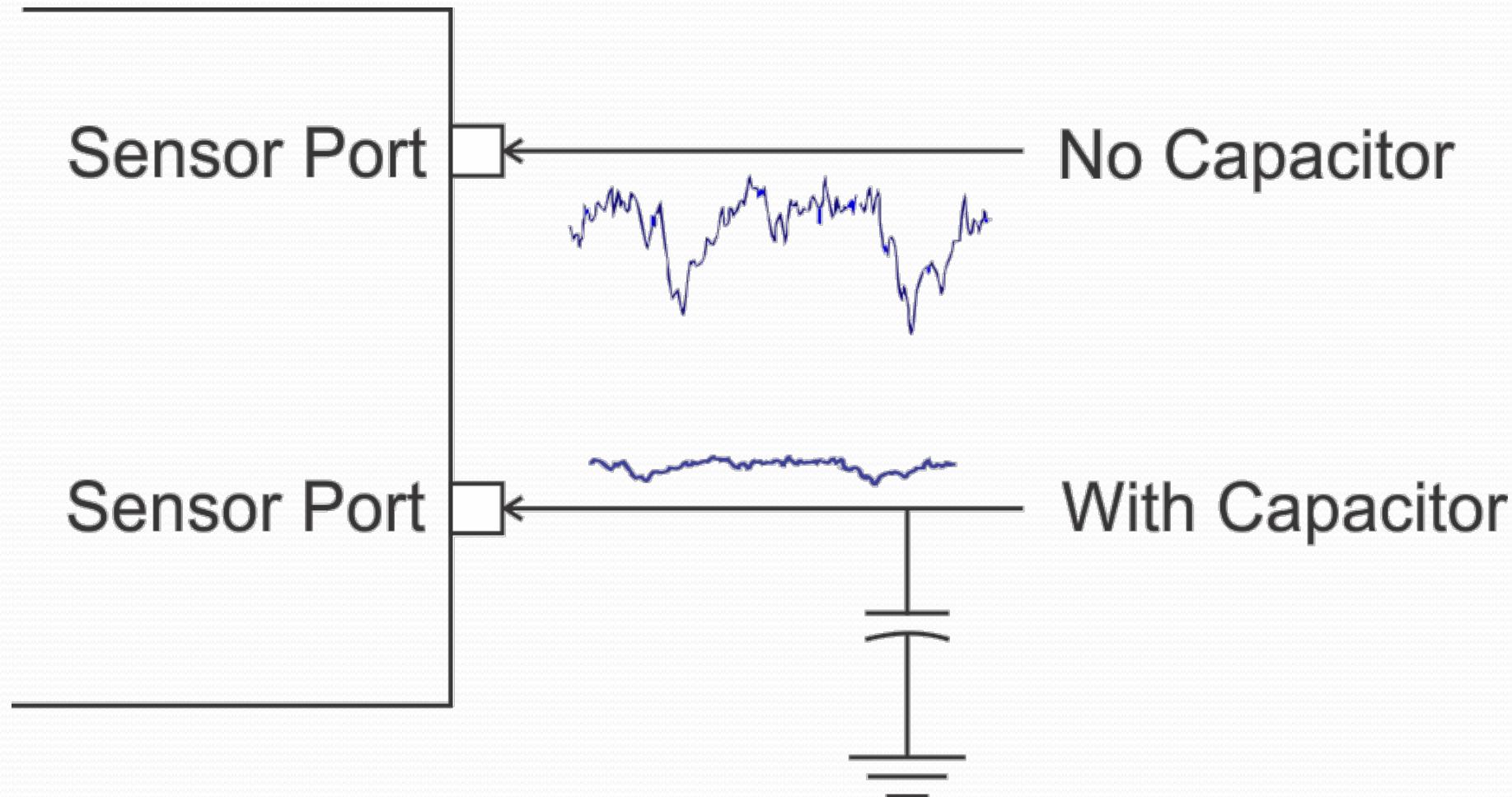

# How do we know the right capacitor size to use?

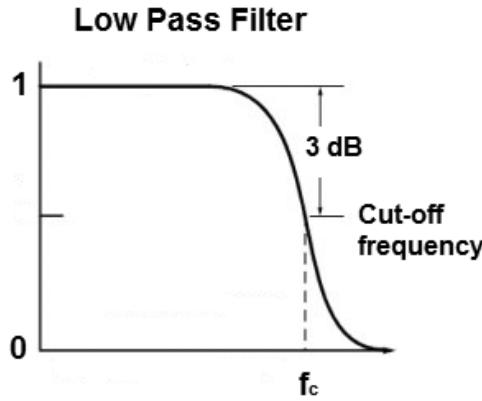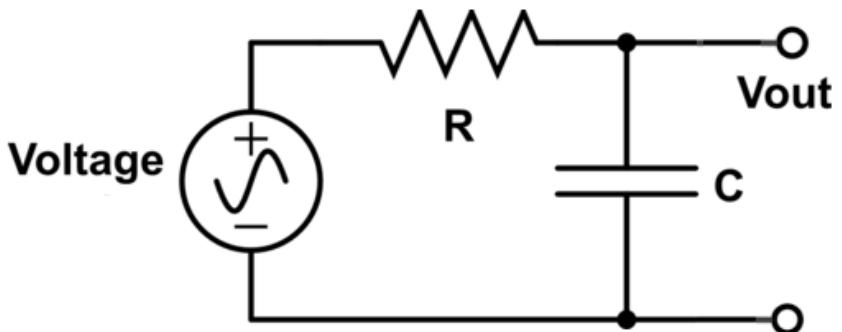- 
1. Trial & error
  2. Calculate the frequency response of a low-pass filter



$$f_c = \frac{1}{2\pi RC}$$

$f_c$  is where the output power (not amplitude) is half of the input.

# Simple Low-Pass Filtering: Software Implementation

---

$$X_n = \frac{wX_{(n-1)} + I}{w + 1}$$

Where


- $X_n$  = The current average value
- $X(n-1)$  = The previous average value
- $I$  = new sensor value
- $w$  = weight

# Example: Small Weight

Limited noise rejection

---

Data Input and Filtered Data

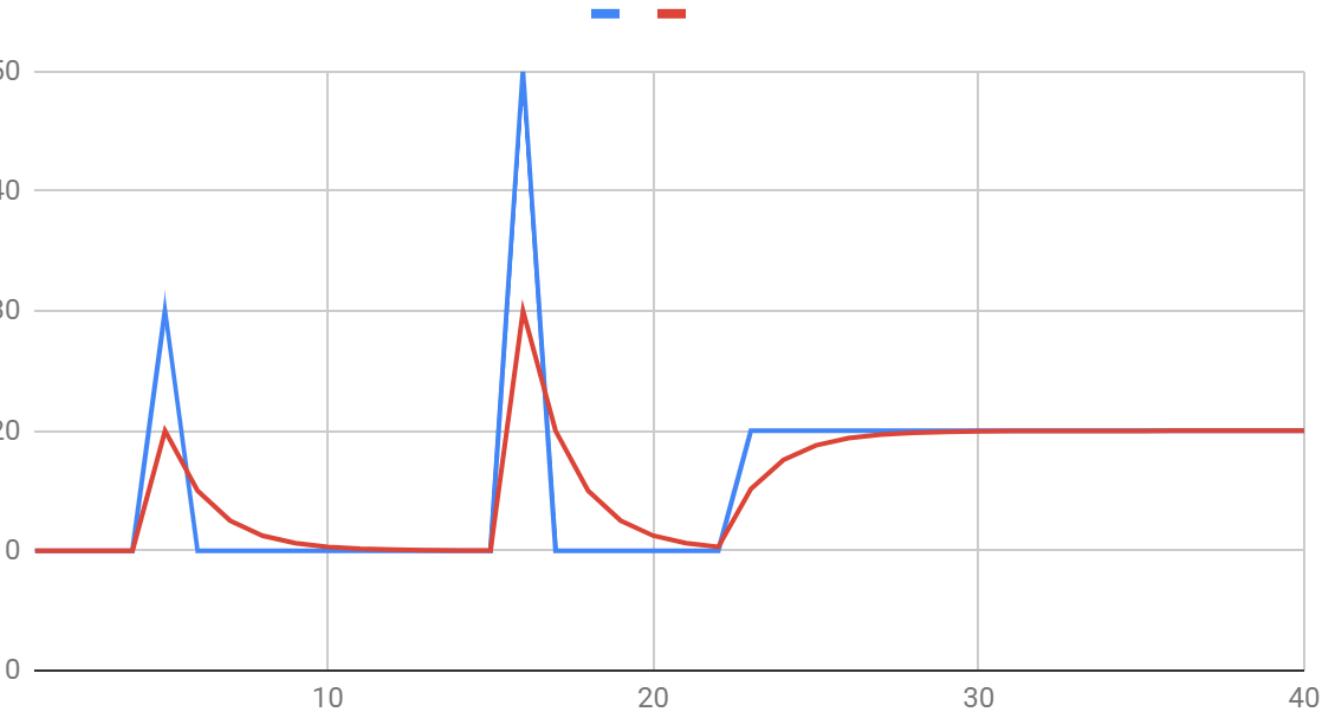


[Open this example](#)

# Example: Higher weight

Better noise rejection, but also causes a delay

-----

Data Input and Filtered Data

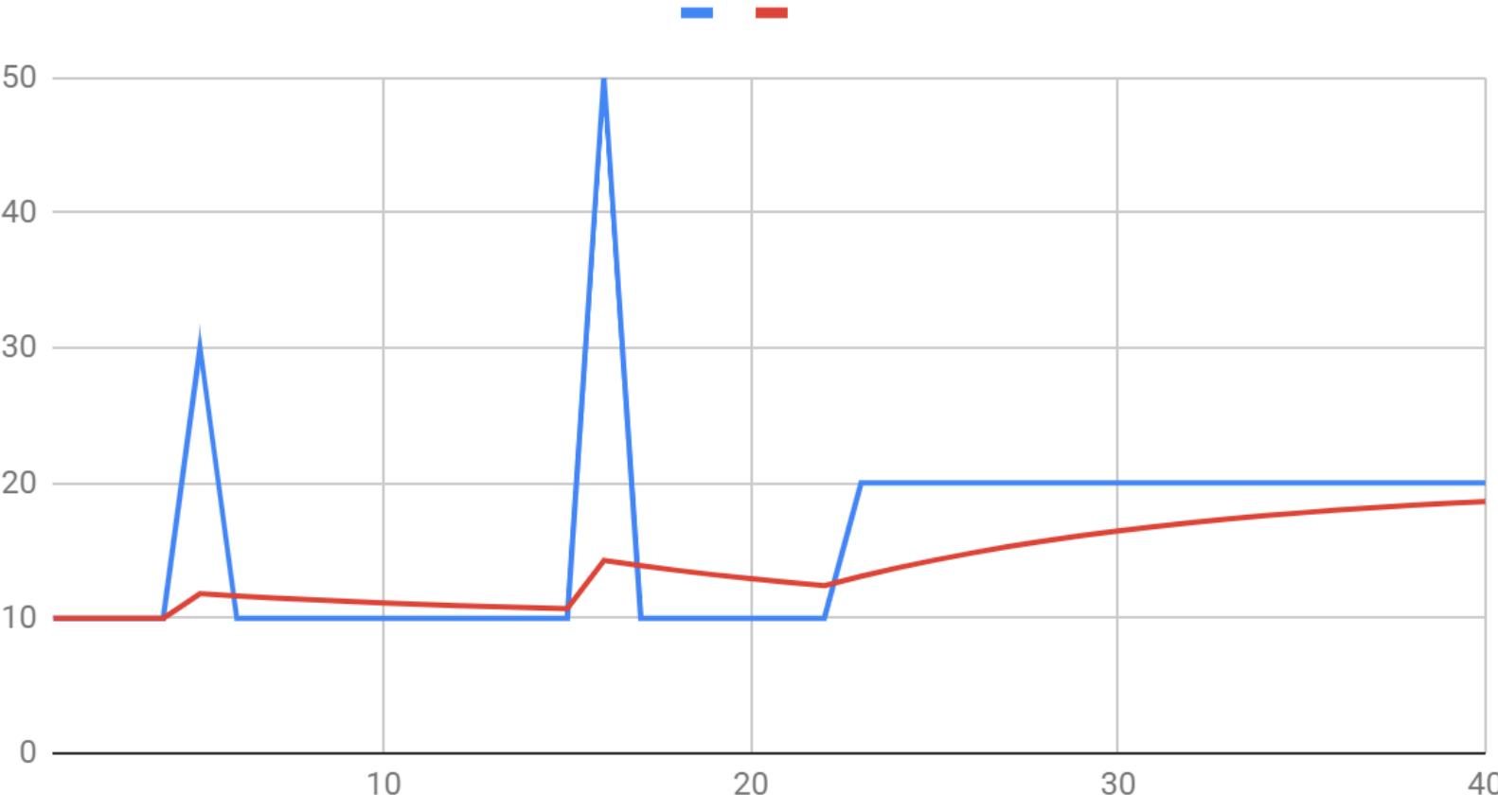


# Digital Interfaces and Basic PIC-C I2C Communication

**Arnan (Roger) Sipitakiat**

Department of Computer Engineering, Chiang Mai University, Thailand
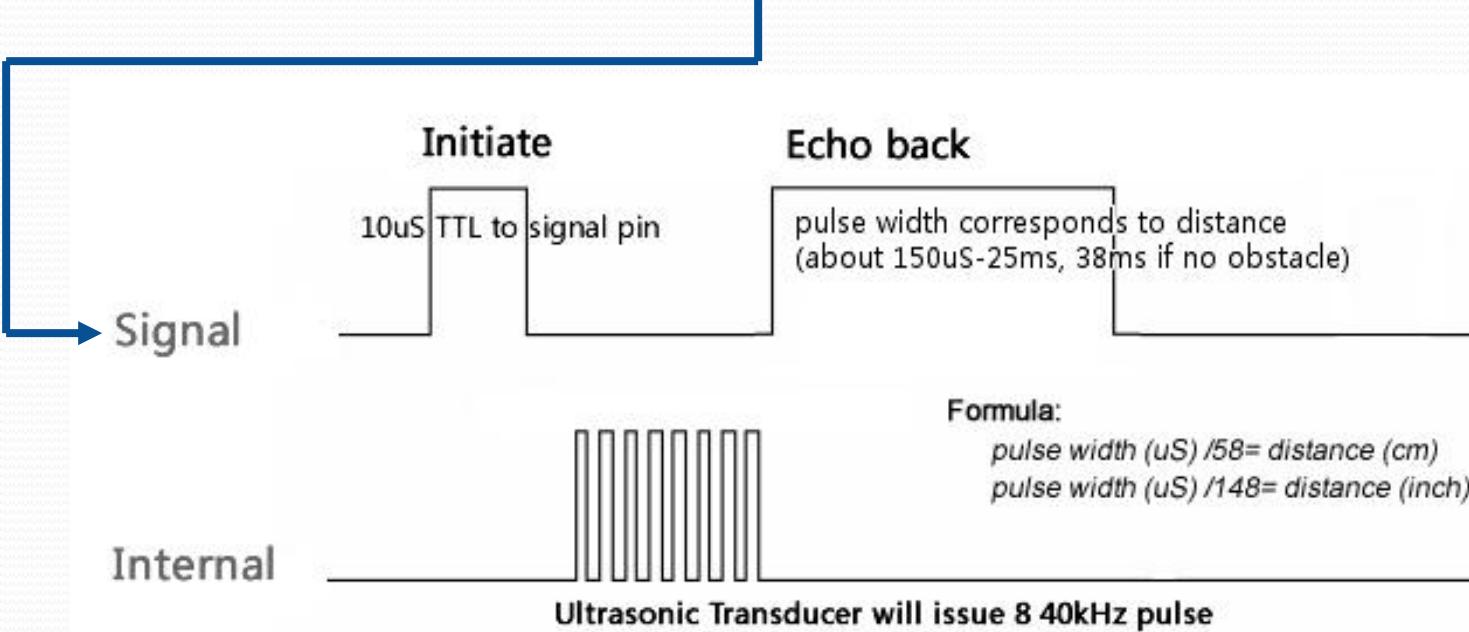
# Why I2C?

Case study of how an Ultrasonic Proximity Sensor works



# Direct Connection to the module

You need to do all the timing yourself




**Implement timing**



# Offload to an I2C Host

Let an I2C host perform the timing

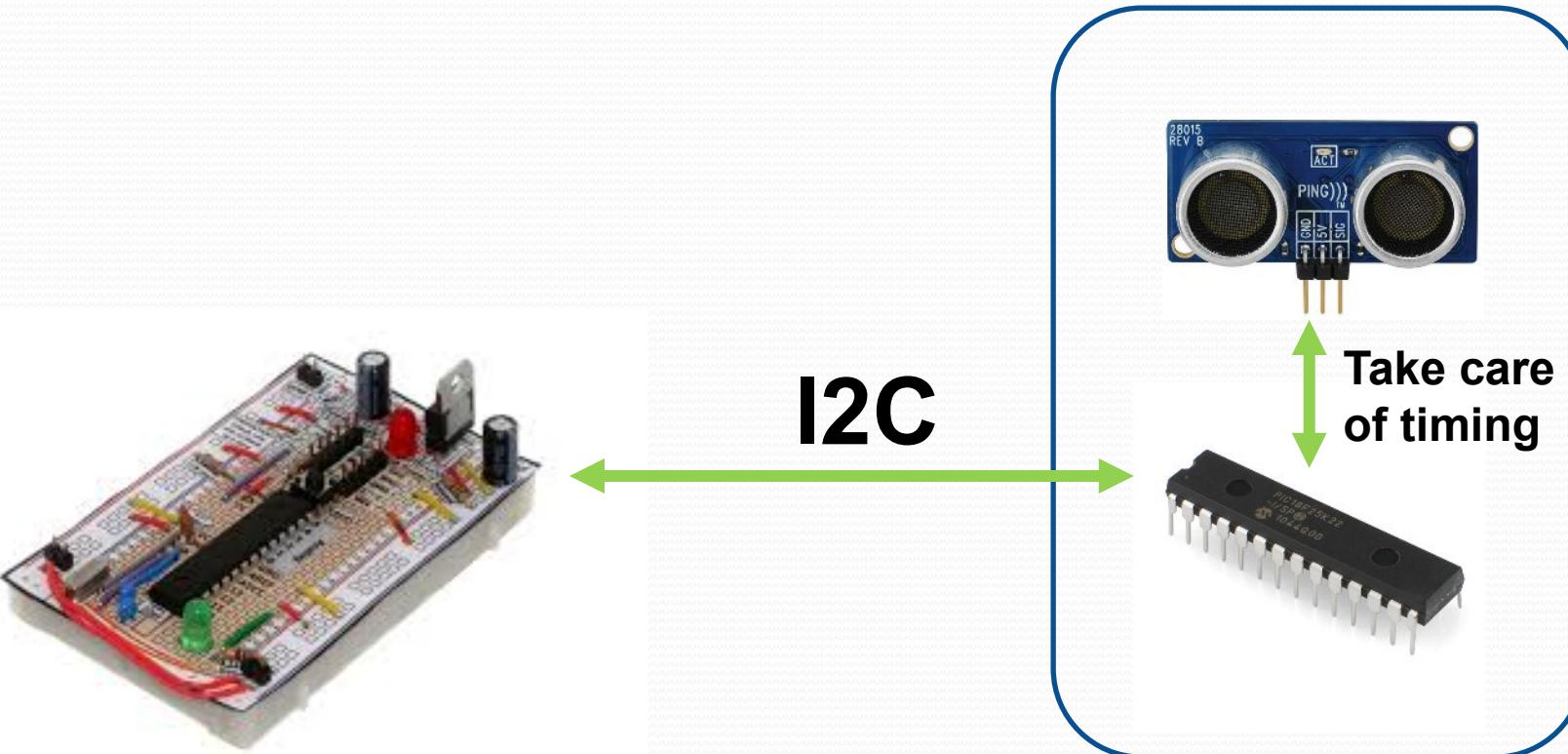

This idea is similar to software abstraction where you create subroutines to hide unnecessary details

# Tradeoffs of offloading

- **Benefits**

- The sensor is simpler to use.
- The main processor is free to do other things.
- More modular.

- **Drawbacks**

- More expensive
- Must be careful of timing problems on the I<sub>2</sub>C host

# Example 2. I<sub>2</sub>C devices on the market



Digital Clock



Barometer




Temperature & RH



Color Sensor




Accelerometer

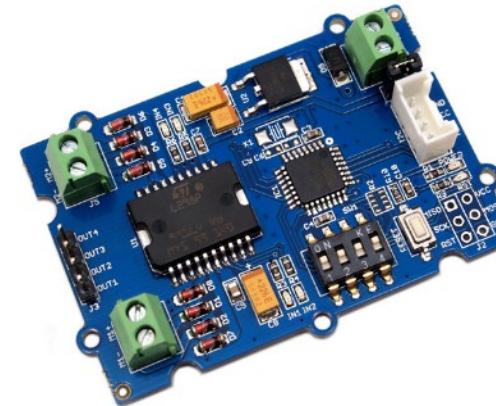

Motor Driver

# Motor Driver Module

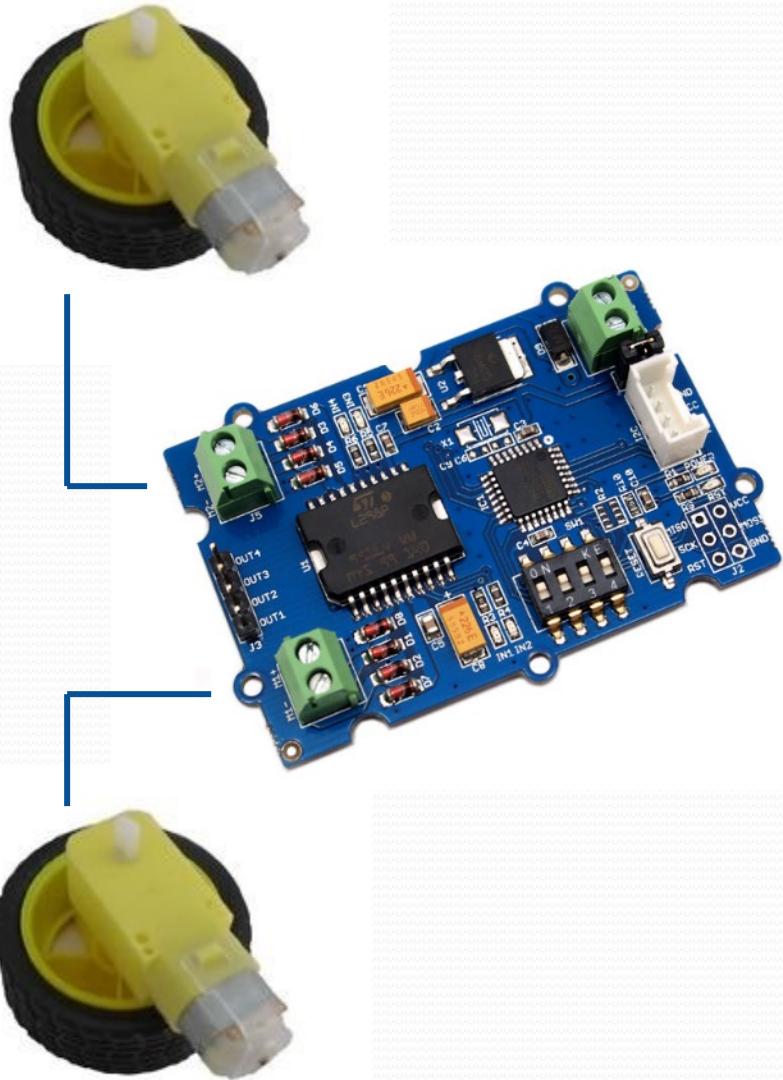

Register Address	Function
0x82	Speed (0-255)
0x84	PWM Frequency
0xA0	Direction (0/1)
0xA1	Select Motor A (0/1)
0xA5	Select Motor B (0/1)

# Clock Module

Module address = 0xD0



**Table 2. Timekeeper Registers**

ADDRESS	BIT 7	BIT 6	BIT 5	BIT 4	BIT 3	BIT 2	BIT 1	BIT 0	FUNCTION	RANGE			
00h	CH	10 Seconds				Seconds				Seconds 00–59			
01h	0	10 Minutes				Minutes				Minutes 00–59			
02h	0	12	10 Hour	10 Hour	Hours				Hours	1–12 +AM/PM 00–23			
		24	PM/ AM										
03h	0	0	0	0	0	DAY			Day	01–07			
04h	0	0	10 Date		Date				Date	01–31			
05h	0	0	0	10 Month	Month				Month	01–12			
06h	10 Year				Year				Year	00–99			
07h	OUT	0	0	SQWE	0	0	RS1	RS0	Control	—			
08h–3Fh									RAM 56 x 8	00h–FFh			

0 = Always reads back as 0.


The DS1307 can be run in either 12-hour or 24-hour mode. Bit 6 of the hours register is defined as the 12-hour or 24-hour mode-select bit. When high, the 12-hour mode is selected. In the 12-hour mode, bit 5 is the AM/PM bit with logic high being PM. In the 24-hour mode, bit 5 is the second 10-hour bit (20 to 23 hours). The hours value must be re-entered whenever the 12/24-hour mode bit is changed.

# Bitwise Operations

# I<sub>2</sub>C Basics

- I<sub>2</sub>C is a Bus. Serial is point-to-point
- Master and Slave pair
  - Master must start the communication
  - Slave can only respond
- Slave has a 8-bit address
  - Bit 0 is reserved for direction control

# Basic I2C Bus Setup

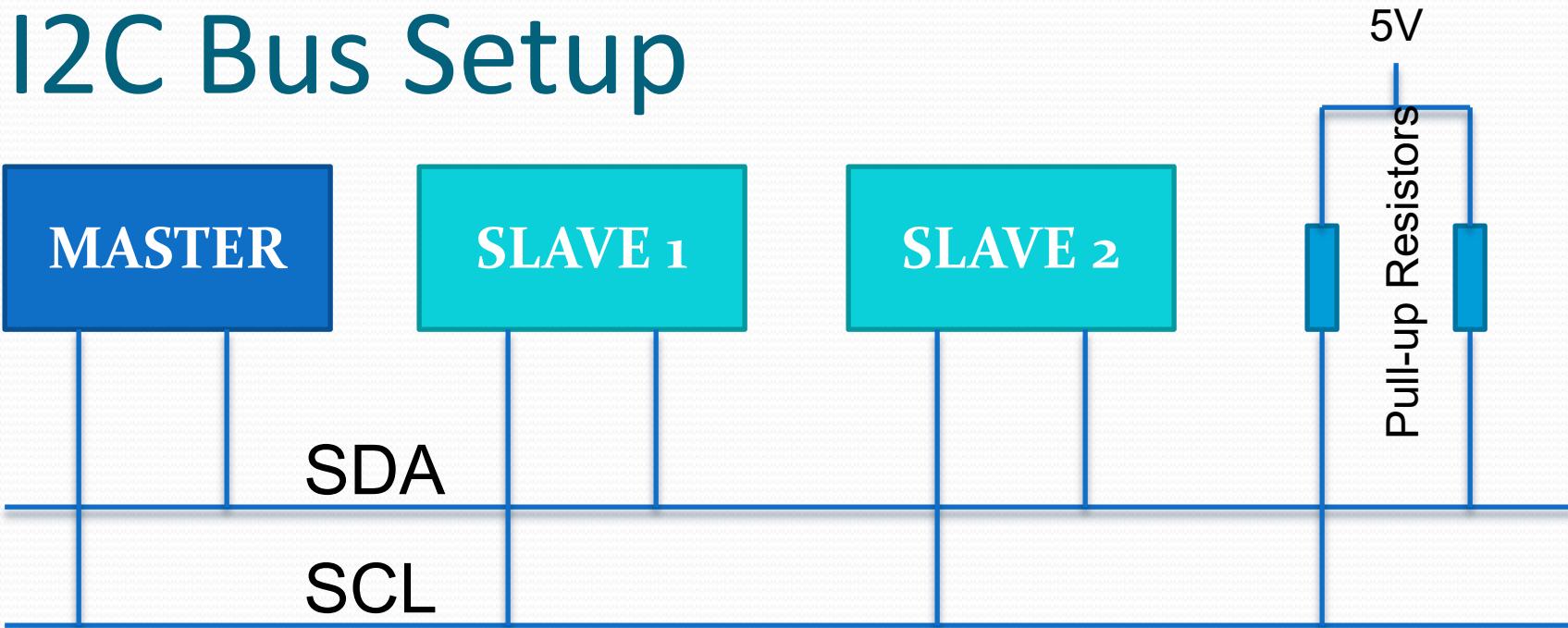

# i2C Commands in PIC-C

Master Only

`I2C_start()`

`I2C_stop()`

Slave Only

`I2C_isr_state()`

Master & Slave

`I2C_read()`

`I2C_write()`

# Sending 1 Byte to Slave

MASTER

SLAVE

I2c\_start()

I2c\_write(slave addr | 0)

I2c\_write(registerAddres  
s)

I2c\_write(value)

I2c\_stop()

Address	Content
0	0
1	0
2	0
3	0
4	0
5	0
6	0
7	0

# Reading 2 bytes from slave

MASTER

SLAVE

I<sub>2</sub>C\_start()

I<sub>2</sub>C\_write(slave addr | 0)

I<sub>2</sub>C\_write(registerAddress)

I<sub>2</sub>C\_start()

I<sub>2</sub>C\_write(slave addr | 1)

Value1 = I<sub>2</sub>C\_read()

Value2 = I<sub>2</sub>C\_read(0)

I<sub>2</sub>C\_stop()

Address	Content
0	0
1	0
2	0
3	0
4	0
5	0
6	0
7	0

Write ค่า 50 ไปยัง Register 5 ของ slave ที่มี address = 100

```
I2c_start();
```

Write ค่า 1000 ไปยัง Register 5 (ใบทับบน), 6 (ใบท์ล่าง) ของ slave ที่มี address = 100

```
I2c_start();
```

# Read ค่าจาก Register 5 ของ slave ที่มี address = 100

```
Int returnValue;  
I2c_start();
```

Read ค่าเซ็นเซอร์ 2 byte จาก Register 5,6 ของ slave ที่มี address  
= 100 และนำมาประกอบกันเป็นค่า int 16 Bit Register 5 = byte บน

Int16 Value;

I2c\_start();

## Example |

# Controlling the Display Module

## Address = 0xB0

Register Address	Function
2	High Byte
3	Low Byte

# Example Program

// i2c1 - Master

```
#use i2c(MASTER, I2C1)
```

```
// Show the number 100 on the screen
I2c_start();
I2c_write(0xB0 | 0); // display module address
I2c_write(2); // show number command
I2c_write(0);
I2c_write(100);
I2c_stop();
```

# Example II

## Reading from the ultrasonic sensor



# What is bitwise operations?

## Logical Operation

3 and 2 = ?

3 && 2 = ?

## Bitwise Operation

3 & 2 = ?

# Bitwise vs Logical Operators

- Logical operators results in “True” or “False” only.

- Examples

- $0b011 \& 0b110 = 0b010$  (bitwise)

- $0b011 \&\& 0b110 = \text{True}$  (logical)

- $\sim 0b010 = 0b101$  (bitwise)

- $\text{!}0b010 = \text{False}$  (logical)

# เลขฐาน 10, 2, และ 16

10 (ฐาน 10) = 0b1010 (ฐาน 2) = 0x0A (ฐาน 16)

ฐาน 2 ใช้สัญลักษณ์ตัว b ส่วน ฐาน 16 ใช้ตัว x

ฐาน 16 หนึ่งหลัก = 4 หลักฐาน 2

0x12 = 0b0001 0010

# Useful Bitwise Operations

# Practice in Python using repl.it



repl.it

# Clock Module




**Table 2. Timekeeper Registers**

ADDRESS	BIT 7	BIT 6	BIT 5	BIT 4	BIT 3	BIT 2	BIT 1	BIT 0	FUNCTION	RANGE
00h	CH	10 Seconds				Seconds				Seconds 00–59
01h	0	10 Minutes				Minutes				Minutes 00–59
02h	0	12	10 Hour	10 Hour	Hours				Hours 1–12 +AM/PM 00–23	1–12 +AM/PM 00–23
		24	PM/ AM							
03h	0	0	0	0	0	DAY				Day 01–07
04h	0	0	10 Date		Date				Date	Date 01–31
05h	0	0	0	10 Month	Month				Month	Month 01–12
06h	10 Year				Year				Year	Year 00–99
07h	OUT	0	0	SQWE	0	0	RS1	RS0	Control	—
08h–3Fh									RAM 56 x 8	00h–FFh

*0 = Always reads back as 0.*

The DS1307 can be run in either 12-hour or 24-hour mode. Bit 6 of the hours register is defined as the 12-hour or 24-hour mode-select bit. When high, the 12-hour mode is selected. In the 12-hour mode, bit 5 is the AM/PM bit with logic high being PM. In the 24-hour mode, bit 5 is the second 10-hour bit (20 to 23 hours). The hours value must be re-entered whenever the 12/24-hour mode bit is changed.

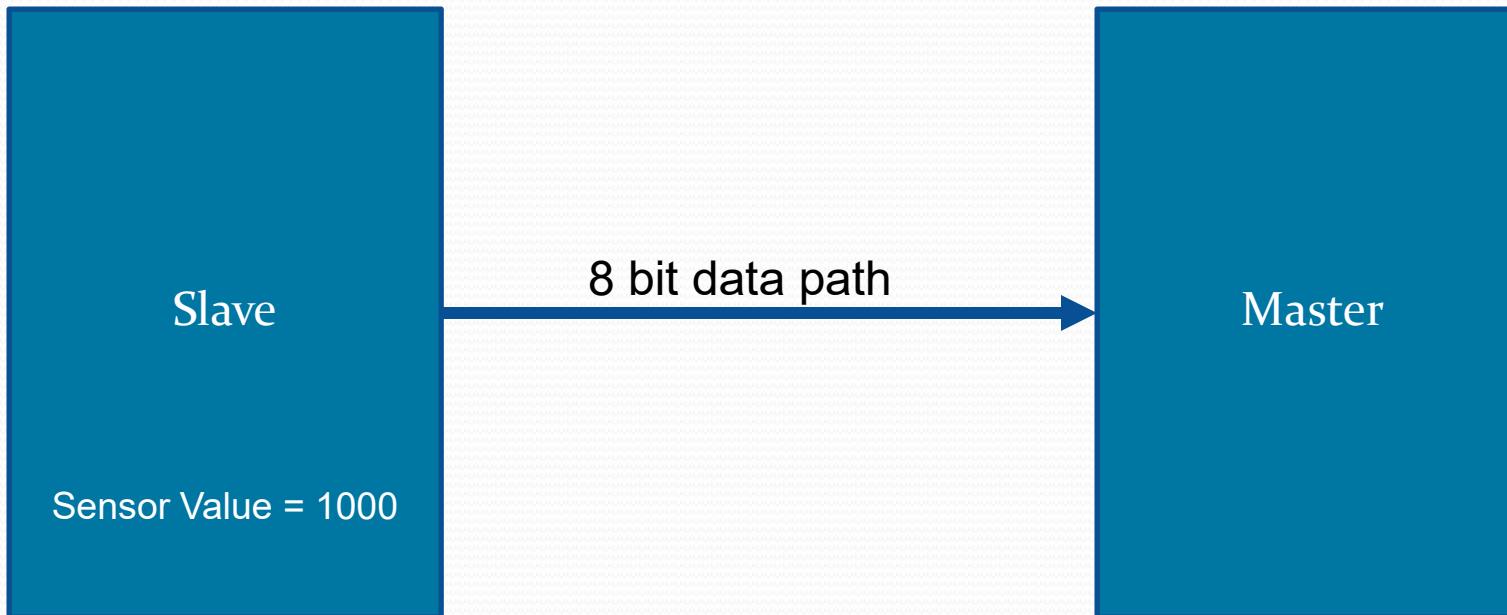ถ้าค่าเซ็นเซอร์ = 1000 (10 bit) จะส่งค่านี้จาก slave ไป master  
ต้องเขียนโปรแกรมอย่างไรถ้าส่งข้อมูลได้ทีละ 1 byte (8 bit)



Write(1000); ???

# ส่งค่า 16 bit ผ่าน bus ขนาด 8 bit โดยใช้ Bitwise Operations

ฝึกส่ง

~~write(1000);~~ ผิด

Write(1000 & 0xFF ); ใบห์ล่าง

Write (1000 >> 8); ใบห์บน

ฝึกรับ


Int16 Value = read() + (read() << 8);

ได้เป็น value =  $232 + (3 \ll 8) = 232 + 768 = 1000$
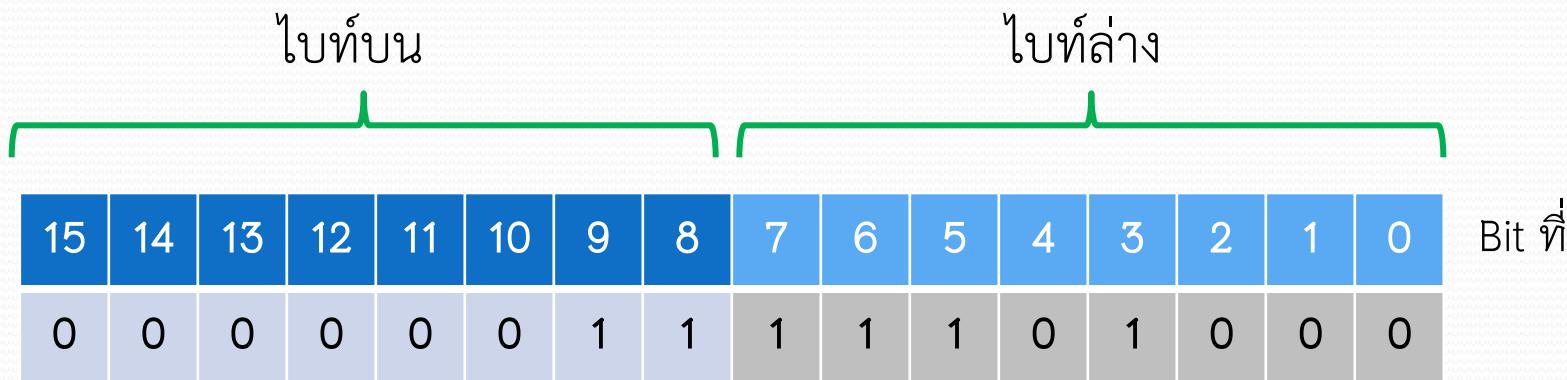
# พิจารณาค่าตัวแปรในรูปเลขฐานต่างๆ

Int16 Data = 1000;

1000 = 0x3E8 (base 16) = 0b1111101000 (base 2)



# Shifting Bits

**Int16 Data = 0x3E8;**

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0	Bit ที่
0	0	0	0	0	0	1	1	1	1	1	0	1	0	0	0	

Data >> 8 = 3

Data << 8 = 0xE8

# Bitwise AND

**Int16 Data = 0x3E8;**

Data & 0xFF00 = 0x300

0x03E8	0	0	0	0	0	0	1	1	1	1	1	0	1	0	0	0
0xFF00	1	1	1	1	1	1	1	1	0	0	0	0	0	0	0	0
0x300	0	0	0	0	0	0	1	1	0	0	0	0	0	0	0	0

&

# Bitwise OR

**Int16 Data = 0x3E8;**

Data | 0xFF00 = 0xFFE8

0x03E8	0	0	0	0	0	0	1	1	1	1	1	0	1	0	0	0
0xFF00	1	1	1	1	1	1	1	1	0	0	0	0	0	0	0	0
0xFFE8	1	1	1	1	1	1	1	1	1	1	1	0	1	0	0	0

# Bitwise NOT

**Int16 Data = 0x3E8;**


**Data = ~Data**

**0x3E8**



---

**0xFC17**

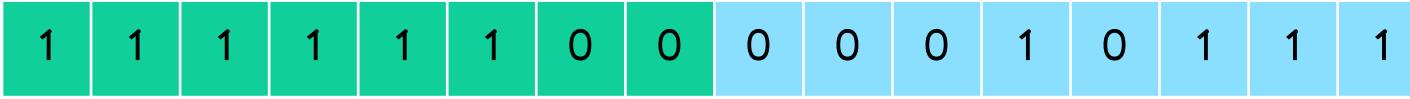

# What is bitwise operations?

## Logical Operation

3 and 2 = ?

3 && 2 = ?

## Bitwise Operation

3 & 2 = ?

# Bitwise vs Logical Operators

- Logical operators results in “True” or “False” only.

- Examples

- $0b011 \& 0b110 = 0b010$  (bitwise)

- $0b011 \&\& 0b110 = \text{True}$  (logical)

- $\sim 0b010 = 0b101$  (bitwise)

- $\text{!}0b010 = \text{False}$  (logical)

# เลขฐาน 10, 2, และ 16

10 (ฐาน 10) = 0b1010 (ฐาน 2) = 0x0A (ฐาน 16)

ฐาน 2 ใช้สัญลักษณ์ตัว b ส่วน ฐาน 16 ใช้ตัว x

ฐาน 16 หนึ่งหลัก = 4 หลักฐาน 2

0x12 = 0b0001 0010

# Useful Bitwise Operations

# Practice in Python using repl.it



repl.it

# Clock Module




**Table 2. Timekeeper Registers**

ADDRESS	BIT 7	BIT 6	BIT 5	BIT 4	BIT 3	BIT 2	BIT 1	BIT 0	FUNCTION	RANGE
00h	CH	10 Seconds				Seconds				Seconds 00–59
01h	0	10 Minutes				Minutes				Minutes 00–59
02h	0	12	10 Hour	10 Hour	Hours				Hours 1–12 +AM/PM 00–23	1–12 +AM/PM 00–23
		24	PM/ AM							
03h	0	0	0	0	0	DAY				Day 01–07
04h	0	0	10 Date		Date				Date	Date 01–31
05h	0	0	0	10 Month	Month				Month	Month 01–12
06h	10 Year				Year				Year	Year 00–99
07h	OUT	0	0	SQWE	0	0	RS1	RS0	Control	—
08h–3Fh									RAM 56 x 8	00h–FFh

*0 = Always reads back as 0.*

The DS1307 can be run in either 12-hour or 24-hour mode. Bit 6 of the hours register is defined as the 12-hour or 24-hour mode-select bit. When high, the 12-hour mode is selected. In the 12-hour mode, bit 5 is the AM/PM bit with logic high being PM. In the 24-hour mode, bit 5 is the second 10-hour bit (20 to 23 hours). The hours value must be re-entered whenever the 12/24-hour mode bit is changed.

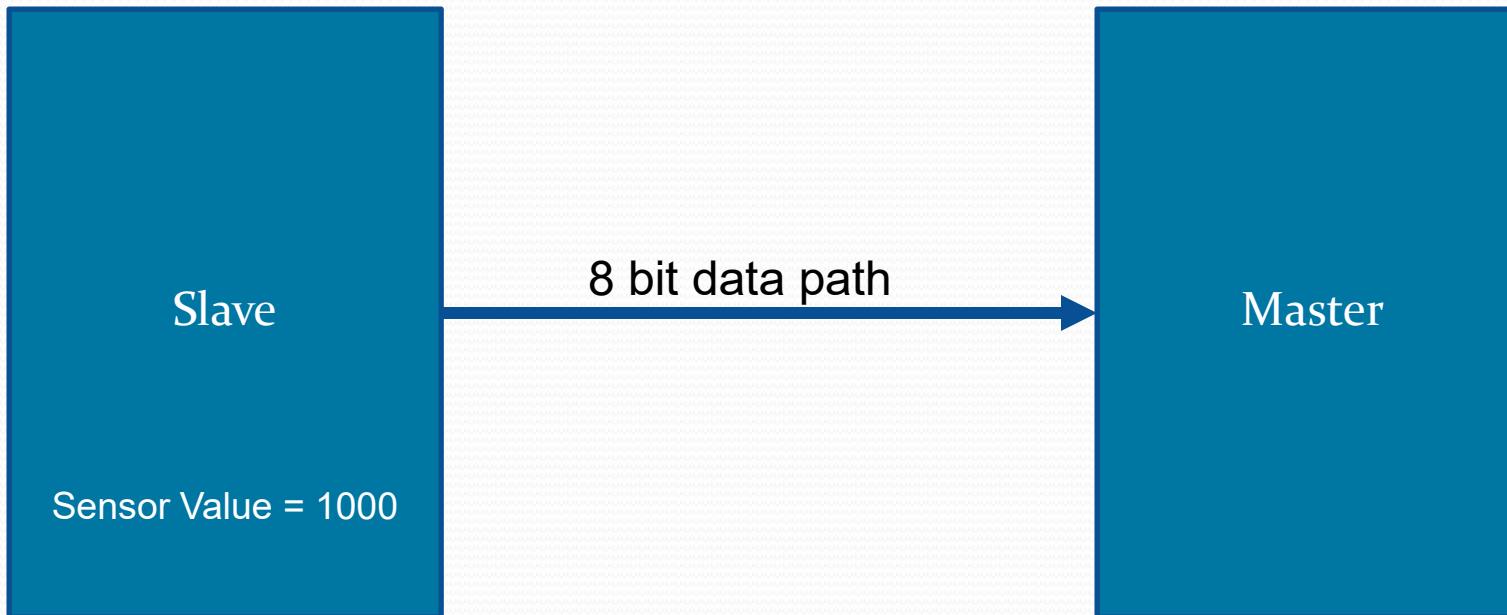ถ้าค่าเซ็นเซอร์ = 1000 (10 bit) จะส่งค่านี้จาก slave ไป master  
ต้องเขียนโปรแกรมอย่างไรถ้าส่งข้อมูลได้ทีละ 1 byte (8 bit)



Write(1000); ???

# ส่งค่า 16 bit ผ่าน bus ขนาด 8 bit โดยใช้ Bitwise Operations

ฝึกส่ง

~~write(1000);~~ ผิด

Write(1000 & 0xFF ); ใบห์ล่าง

Write (1000 >> 8); ใบห์บน

ฝึกรับ


Int16 Value = read() + (read() << 8);

ได้เป็น value =  $232 + (3 \ll 8) = 232 + 768 = 1000$
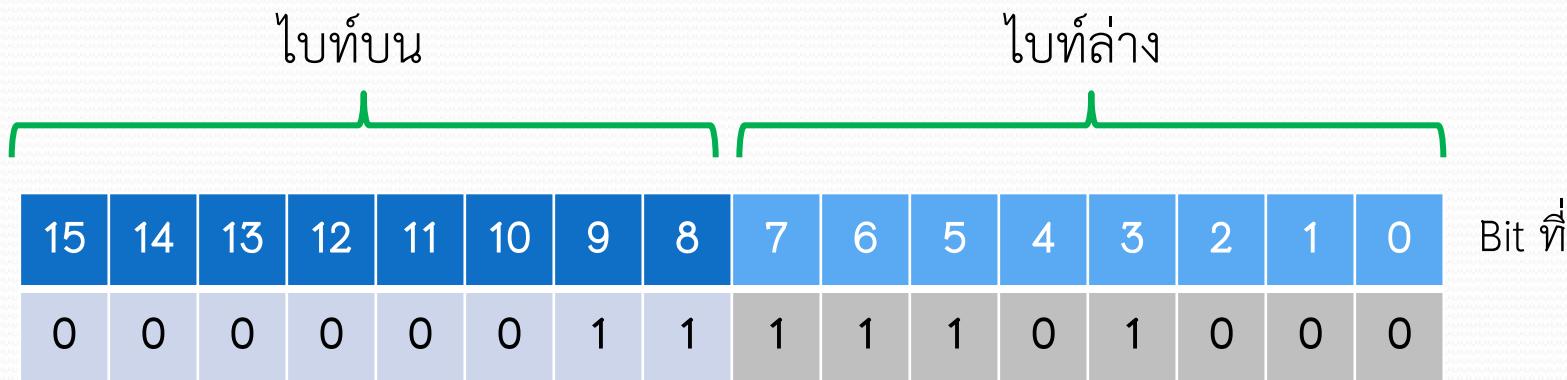
# พิจารณาค่าตัวแปรในรูปเลขฐานต่างๆ

Int16 Data = 1000;

1000 = 0x3E8 (base 16) = 0b1111101000 (base 2)



# Shifting Bits

**Int16 Data = 0x3E8;**

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0	Bit ที่
0	0	0	0	0	0	1	1	1	1	1	0	1	0	0	0	

Data >> 8 = 3

Data << 8 = 0xE8

# Bitwise AND

**Int16 Data = 0x3E8;**

**Data & 0xFF00 = 0x300**

0x03E8	0	0	0	0	0	0	1	1	1	1	1	0	1	0	0	0
0xFF00	1	1	1	1	1	1	1	1	0	0	0	0	0	0	0	0
0x300	0	0	0	0	0	0	1	1	0	0	0	0	0	0	0	0

&

# Bitwise OR

**Int16 Data = 0x3E8;**

Data | 0xFF00 = 0xFFE8

0x03E8	0	0	0	0	0	0	1	1	1	1	1	0	1	0	0	0
0xFF00	1	1	1	1	1	1	1	1	0	0	0	0	0	0	0	0
0xFFE8	1	1	1	1	1	1	1	1	1	1	1	0	1	0	0	0

# Bitwise NOT

**Int16 Data = 0x3E8;**


**Data =  $\sim$ Data**

**0x3E8**



---

**0xFC17**

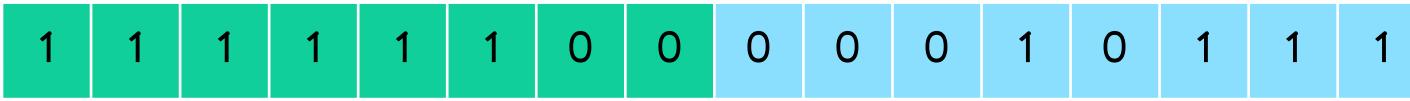


# 1. PWM คืออะไร?

การณีศึกษา

สมมุติว่าต้องการควบคุมความเร็วของมอเตอร์

จะต้องออกแบบวงจรอย่างไร?

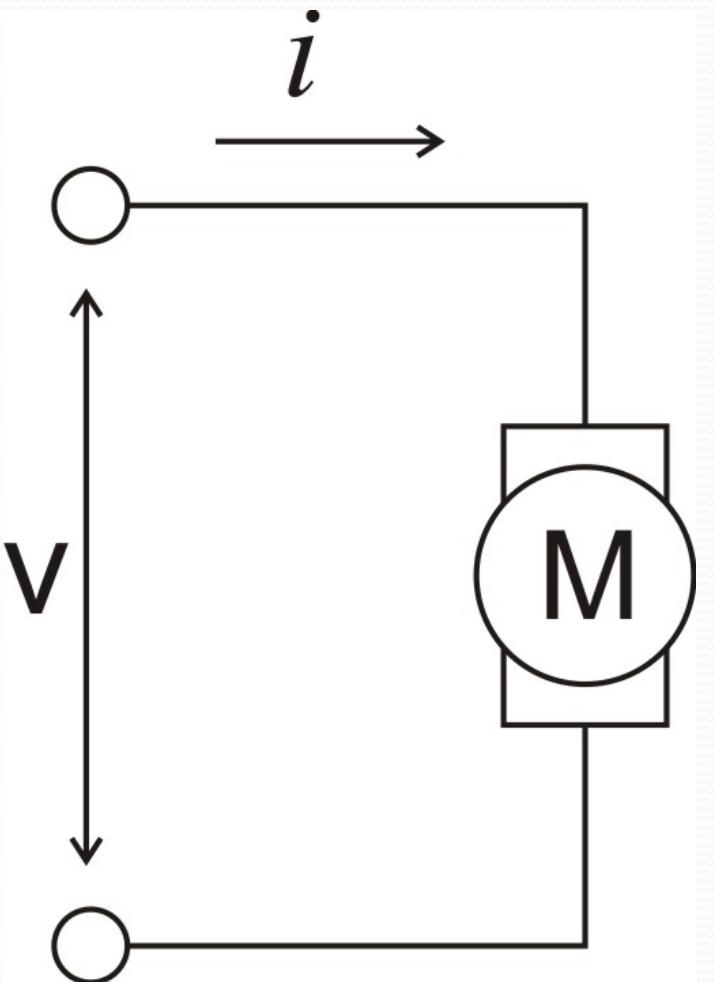


ตามหลักการทั่วไป

ความเร็วการหมุนขึ้นอยู่กับกำลังไฟฟ้า  
ที่ป้อนให้กับมอเตอร์ ซึ่ง

$$\text{Power} = I \times V$$

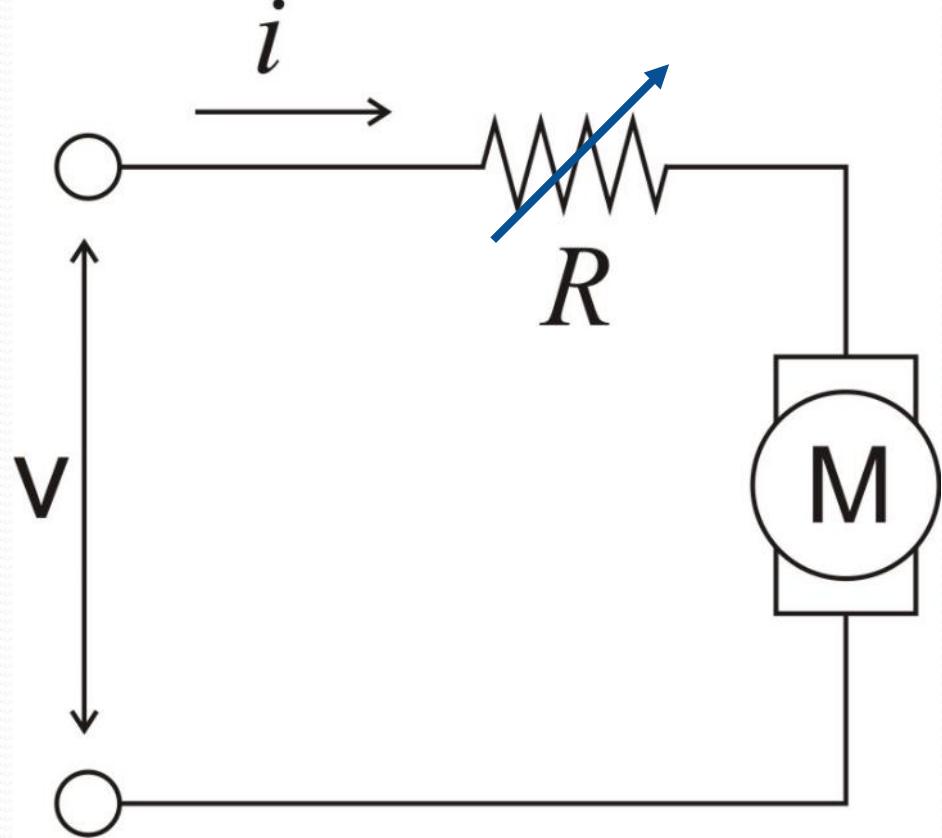ซึ่งหากความต่างศักดิ์คงที่  
สิ่งที่ต้องเปลี่ยนคือกระแส




วิธีหนึ่งที่ทำได้คือควบคุมกระแสด้วยตัวต้านทาน  
หรือตัวต้านทานปรับค่าได้ (Potentiometer หรือ POT)

แต่การเปลี่ยนค่าความต้านทานมักทำไม่สะดวกนัก  
โดยเฉพาะเมื่อต้องการควบคุมผ่านโปรแกรม

นอกจากนั้นโหลดที่ต้องใช้กระแสสูงก็มักทำให้เกิด  
ความร้อนขึ้นที่ตัวต้านทานสูง

# Pulse Width Modulation (PWM)

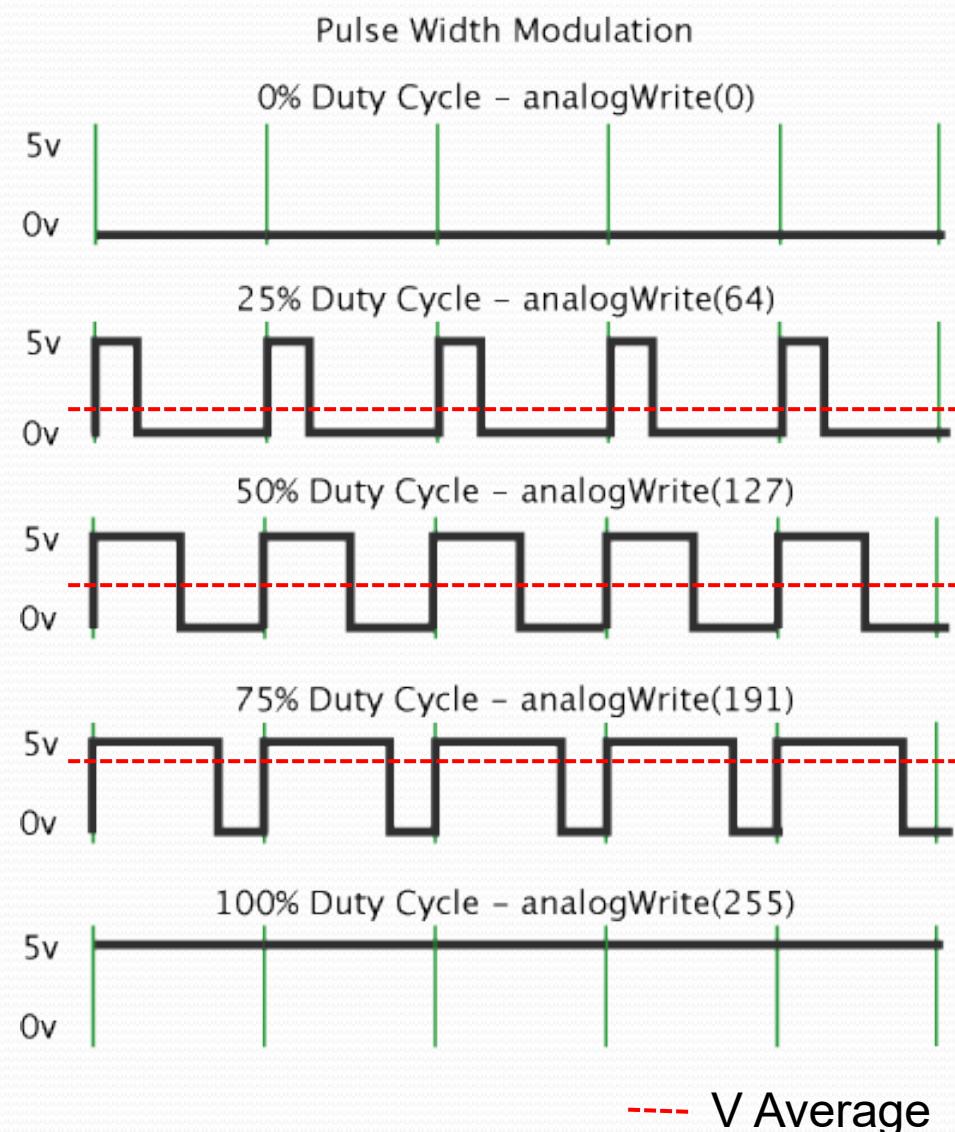

คือการสร้าง Pulse ที่ความถี่สูง\*  
มีเวลาติดและดับแปรผันตามระดับพลังงานที่  
ต้องการจะส่งออกไปยังโหลด

เป็นทางออกที่ได้รับความนิยม เพราะ


- ไม่ต้องแก้ไขวงจร
- ปรับพลังงานผ่านโปรแกรมได้

\* ค่าเป็นเท่าไหร่แล้วแต่งาน
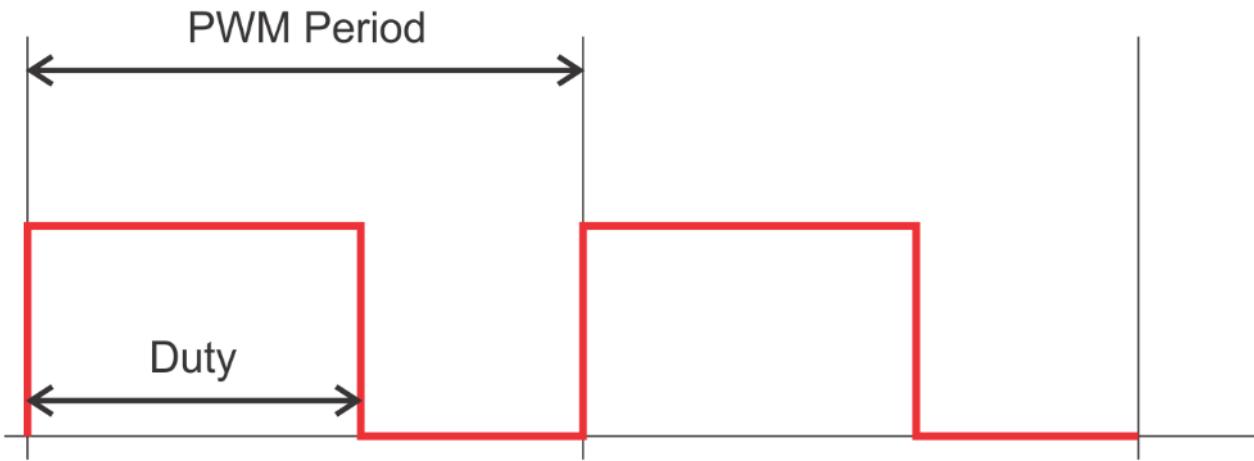
# PWM Parameters

คุณสมบัติของ PWM ที่สำคัญคือ

- คาบ มีหน่วยเป็นเวลา
- Duty มีหน่วยเป็นเปอร์เซ็นต์



Period unit = time (e.g. ms)

Duty unit = % (0 to 100)

## 2. การใช้งาน PWM ในระบบสมองกลฝังตัว

2.1 Power - ใช้ควบคุมพลังงานที่ส่งไปยังโหลด

2.2 Signal – ใช้รับและส่งสัญญาณดิจิทัล


2.3 Digitize – แปลงค่าสัญญาณ อนาล็อก กับ ดิจิทัล

## 2.1 Power - ใช้ควบคุมพลังงานที่ส่งไปยังโหลด


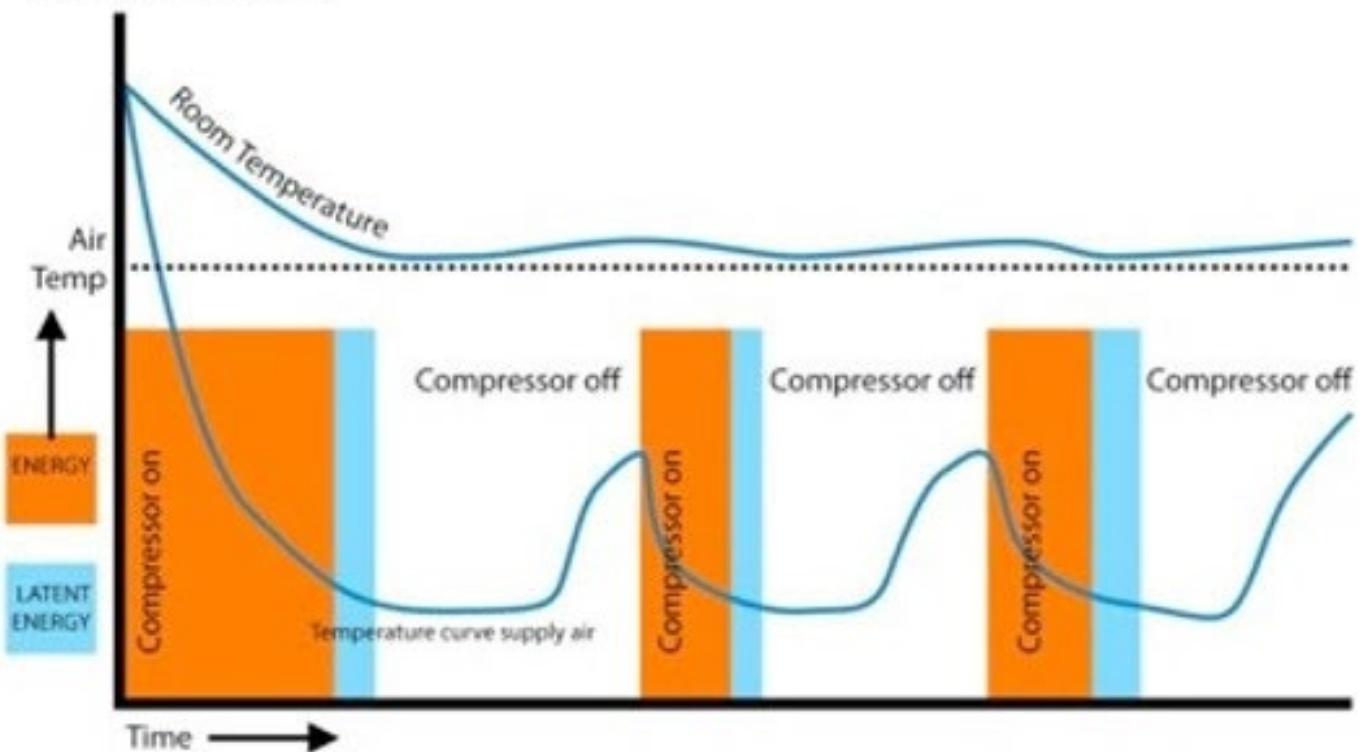
# เครื่องปรับอากาศ (แอร์)

- Compressor ทำงานเมื่อต้องการลดอุณหภูมิ
- ค่าบและ Duty การทำงานของ Compressor เป็นเท่าใด?




กราฟสีเทาแสดงเวลาติด/ดับของ compressor
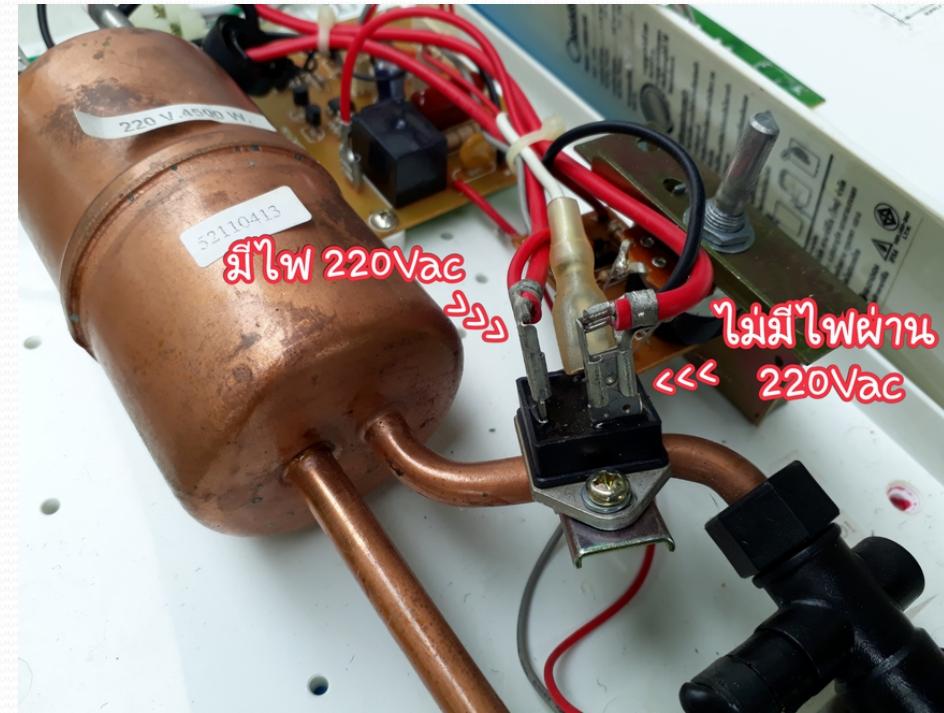
# เครื่องทำน้ำอุ่น



- Triac ควบคุมการเร่งหรือไฟ
- ทำงานเท่ากับความถี่ของไฟบ้าน (50Hz)



# ค่าการทำงานของ PWM ควรเป็นเท่าใด

ให้ดูที่ response time ของ Output นั้นๆ

- เตาแม่เหล็กไฟฟ้า

Response ของอุณหภูมิเป็นหน่วยวินาที ดังนั้นค่า PWM ~15-30 วินาที

- เครื่องปรับอากาศ

Response อุณหภูมิห้องหน่วยเป็นนาที ดังนั้นค่า PWM ~1+ นาที

- หม้อทำน้ำอุ่น

ใช้ Triac ควบคุมไฟ AC ที่ความถี่ 50Hz


- LED?

Response ของแสงหน่วยเป็น ? ดังนั้นค่า PWM ควรเป็น ?

# การออกแบบวงจรควบคุมที่เหมาะสมกับงานที่ต้องการ



Transistor (for DC)

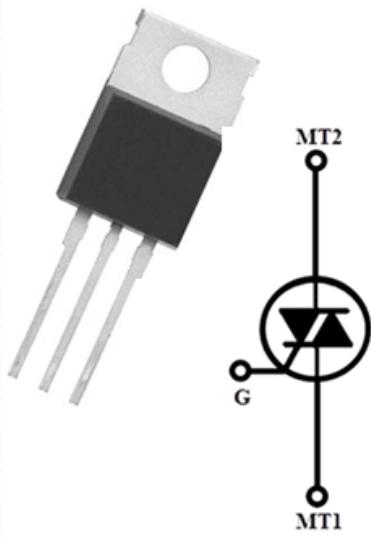

Triac (for AC)



Relay (DC/AC)

# อายุการใช้งาน Relay




สมมุติอย่างอายุการใช้งาน 100,000 operations

ถ้าใช้กับ PWM ที่มีคาบ = 10 Hz


อายุการใช้งานของ relay จะนานเท่าใด?

$$\text{คำตอบ: } 100,000 / 10 = 10,000 \text{ วินาที} = 2.78 \text{ ชม}$$

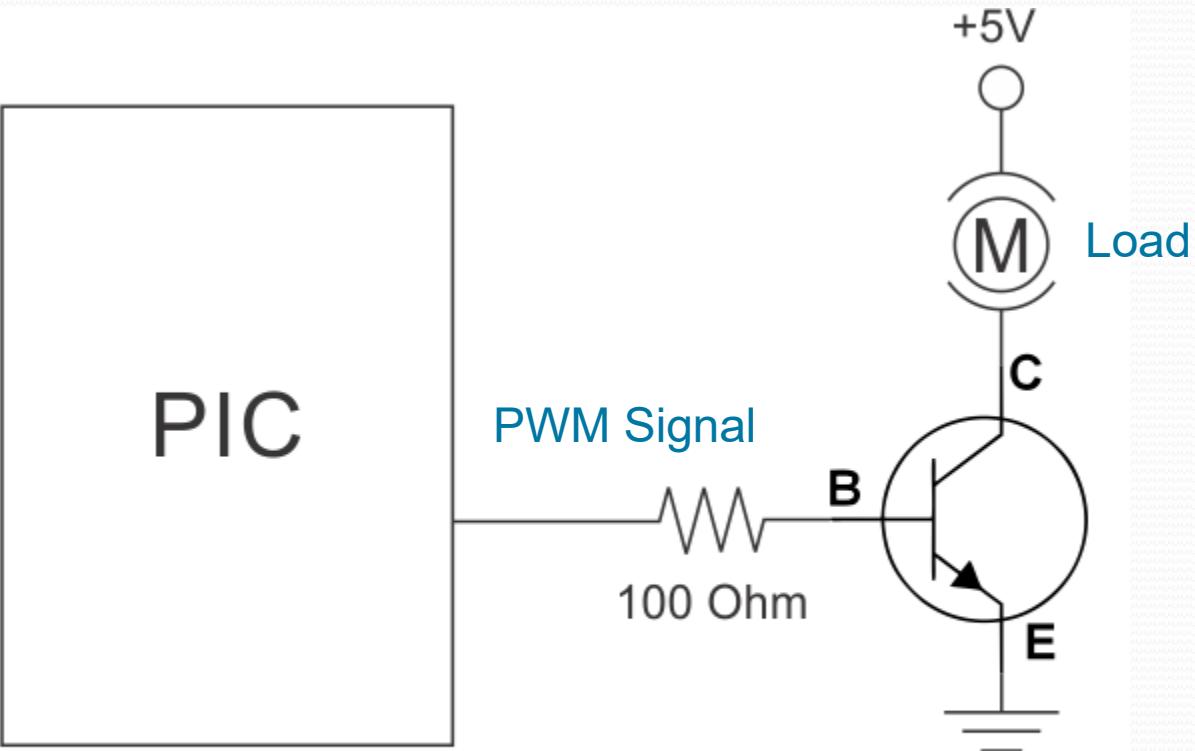
Transistor มีอายุการใช้งานนานมาก แต่มีข้อจำกัดอย่างอื่น เช่น กระแส, ความไว


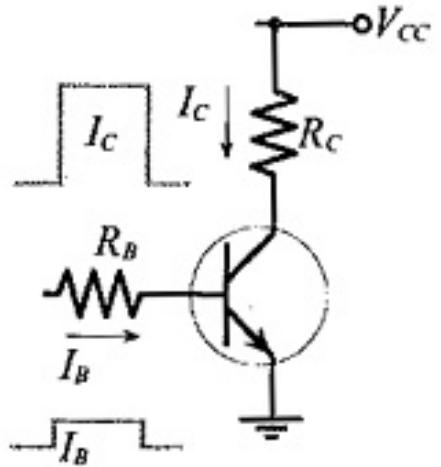
# ตัวอย่างข้อจำกัดในการสร้าง PWM ของ Transistor



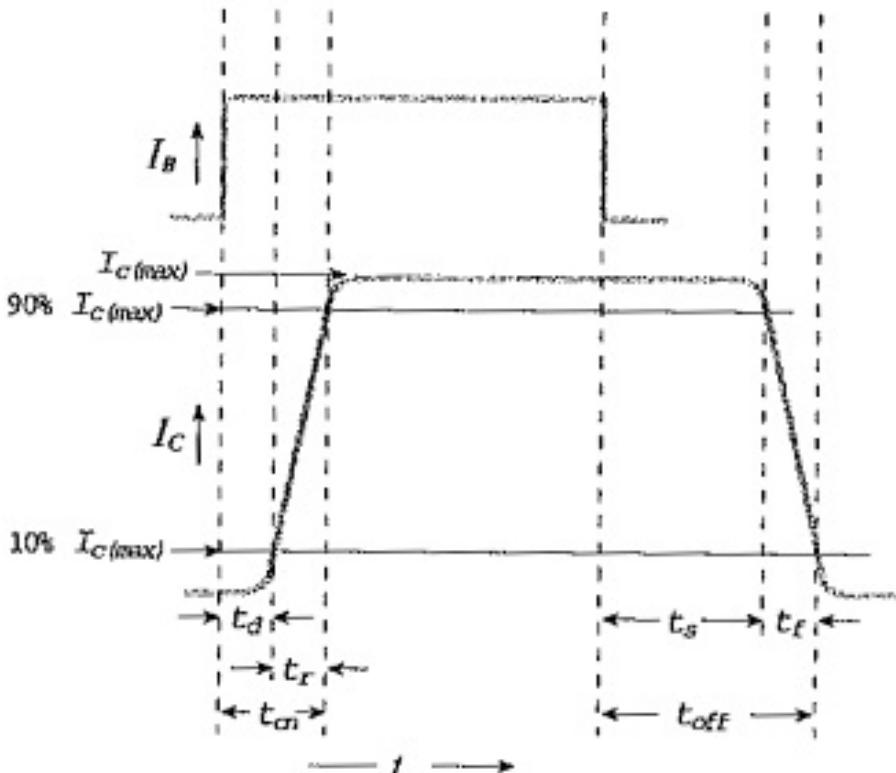(a) Transistor base and collector currents



(b) Current waveform relationships

$T_d$  = Delay Time

$T_r$  = Rising Time

$T_s$  = Storage Time

$T_f$  = Falling Time

# Case Study: NPN 2N3904 Transistor

## SWITCHING CHARACTERISTICS

Delay Time	$(V_{CC} = 3.0 \text{ Vdc}, V_{BE} = 0.5 \text{ Vdc}, I_C = 10 \text{ mA}, I_{B1} = 1.0 \text{ mA})$	$t_d$	-	35	ns
Rise Time		$t_r$	-	35	ns
Storage Time	$(V_{CC} = 3.0 \text{ Vdc}, I_C = 10 \text{ mA}, I_{B1} = I_{B2} = 1.0 \text{ mA})$	$t_s$	-	175	ns
Fall Time		$t_f$	-	200	ns

$$\begin{aligned}\text{Pulse ที่สั้นที่สุด} &= \text{Rise Time} + \text{Storage Time} + \text{Fall Time} \\ &= 35 + 200 + 50 = 285 \text{ ns}\end{aligned}$$

ถ้าสมมุติว่า PWM ที่ต้องการมี 100 ระดับ แสดงว่า 285 ns คือ 1% ของความ  
ดังนั้นความเท่ากัน  $285 \times 100 = 28,500 \text{ ns}$  หรือ  $35.088 \text{ KHz}$

## 2.2 Signal – ใช้ PWM รับและส่งสัญญาณดิจิทัล




Servo Motor ใช้ PWM เป็น Input  
กำหนดตำแหน่งของมอเตอร์





Ultrasonic Proximity Sensor  
ส่งค่าระยะที่วัดได้ออกมาเป็น PWM



# Servo Motor Control

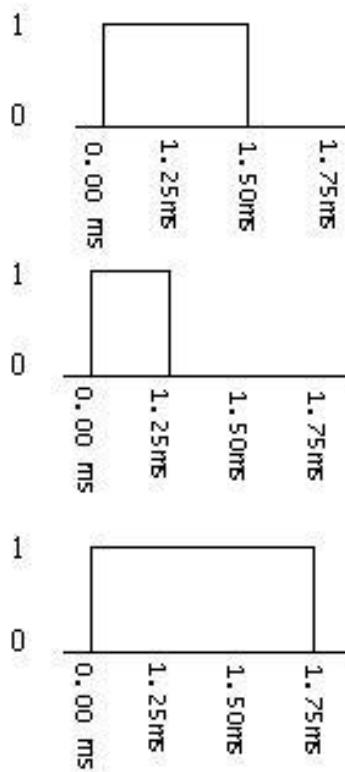

1.50 ms: Neutral

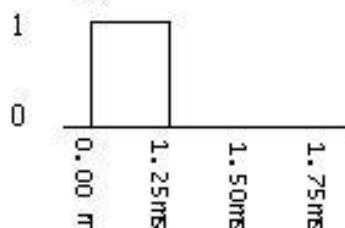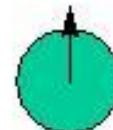



1.25 ms: 0 degrees

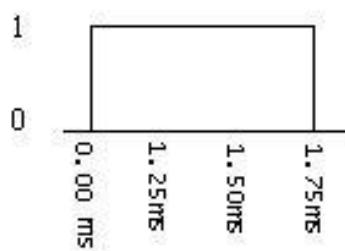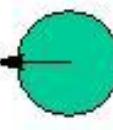


1.75 ms: 180 degrees



# Ultrasonic Proximity Signal

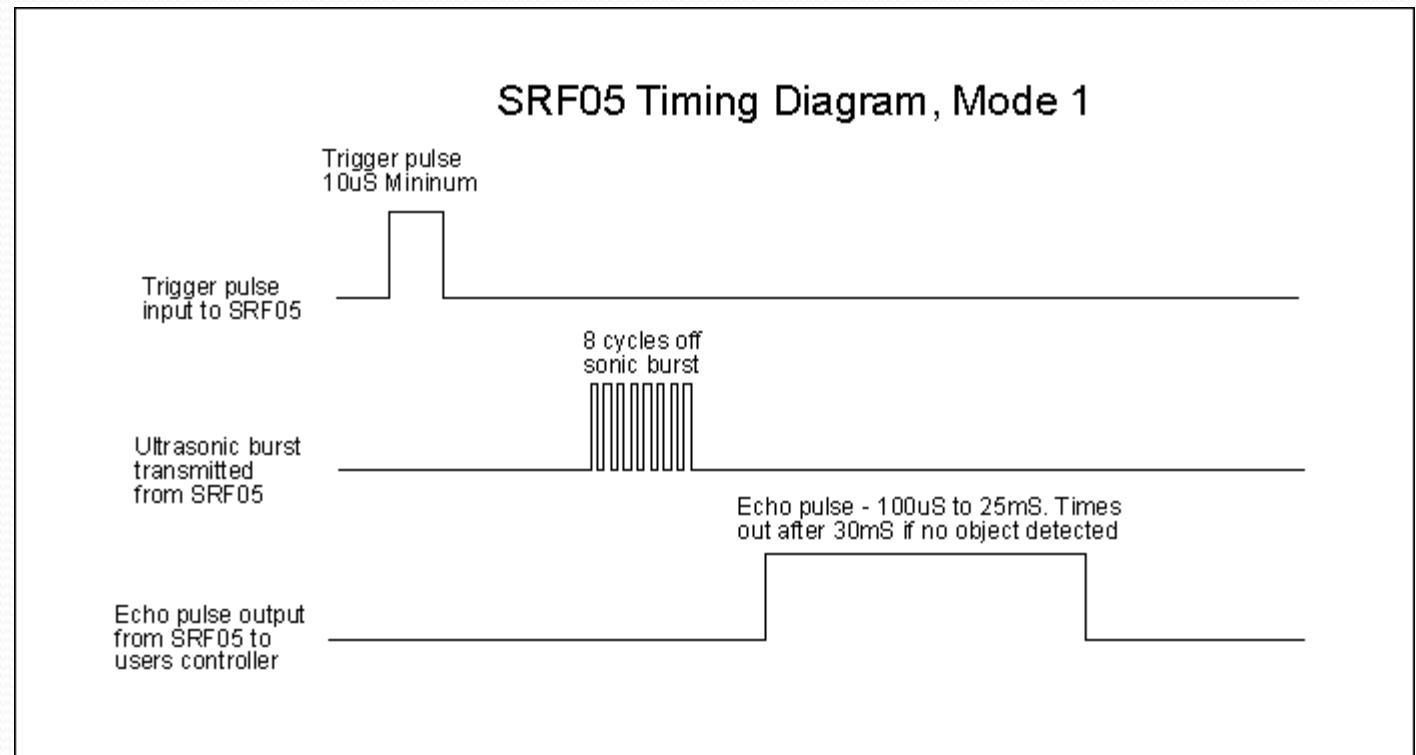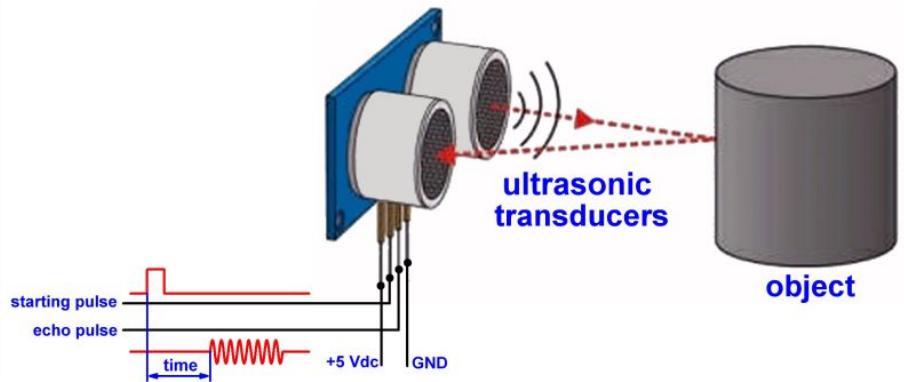

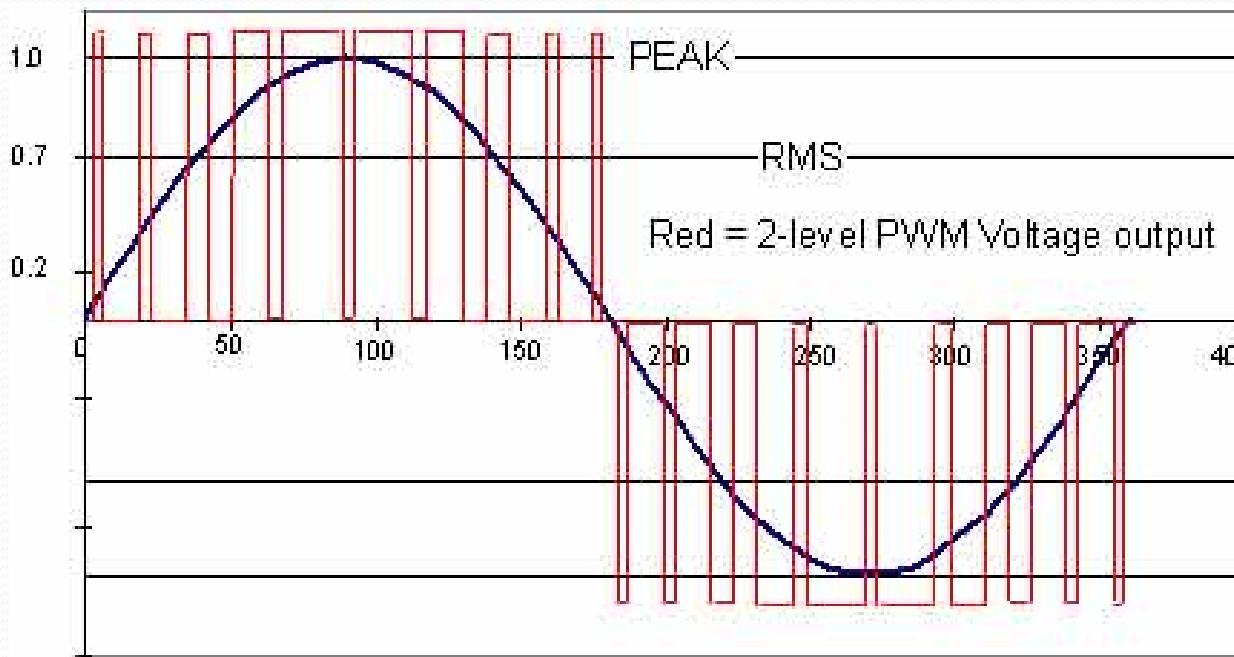
## 2.3 Digitize – แปลงค่าสัญญาณ อนาล็อก กับ ดิจิทัล



ตัวอย่างการแปลงสัญญาโนนาล็อกเป็น  
ดิจิทัลโดยใช้ PWM

# Live Demo

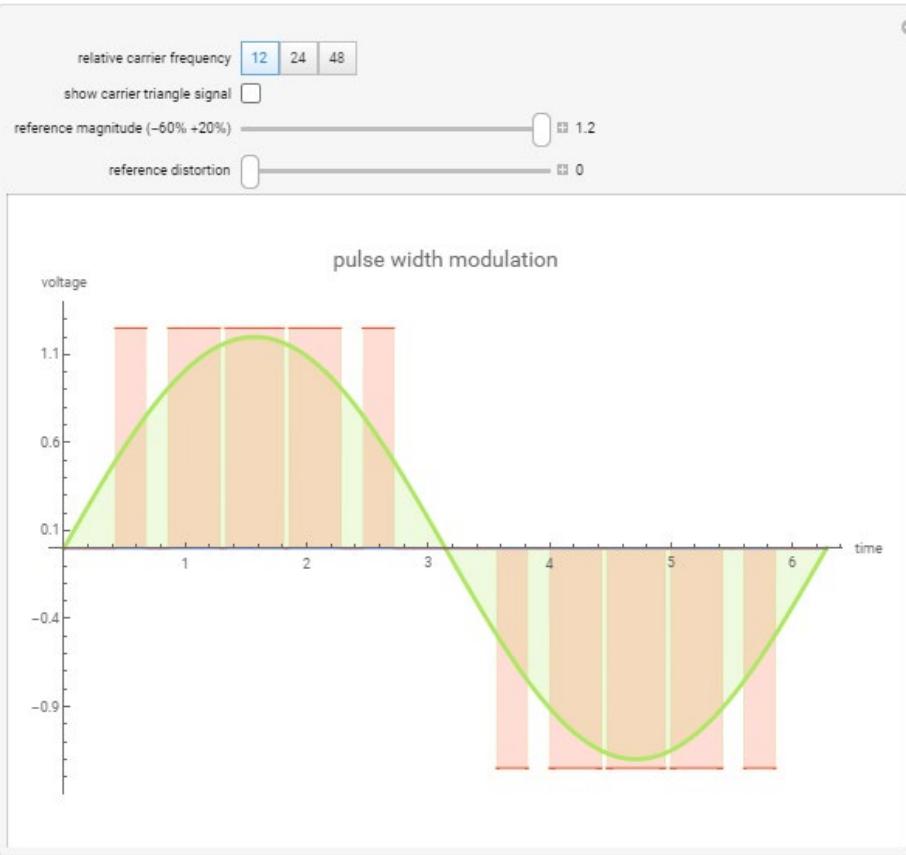

<https://demonstrations.wolfram.com/PulseWidthModulationPrinciple>